

# Chapter 12

## Uncoupled Converter and Extra Element Theorem

# Chapter Outline

---

DC Power Distribution System

Uncoupled Converter

Power Stage Dynamics of Uncoupled Converter

Control Design of Uncoupled Converter


Coupled Converters and Middlebrook's Extra Element Theorem

Load-Coupled Converter

Source-Coupled Converter


Middlebrook's Feedback Theorem
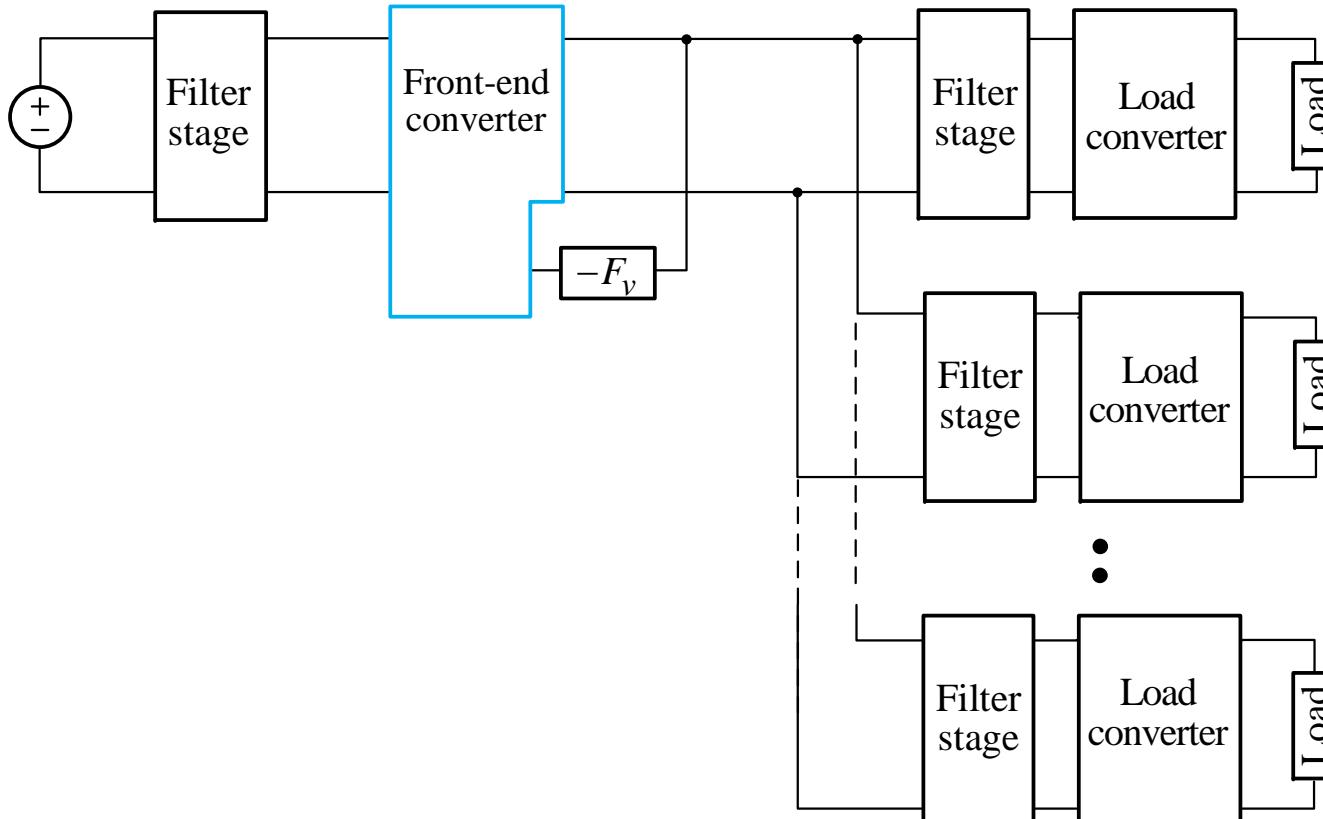
# DC Power Distribution System for Computers




- Cascaded and paralleled converters and filter stages for efficient and reliable power conversion
- Intermediate line filters to meet regulatory EMI standards
- Separate filter stage for each converter
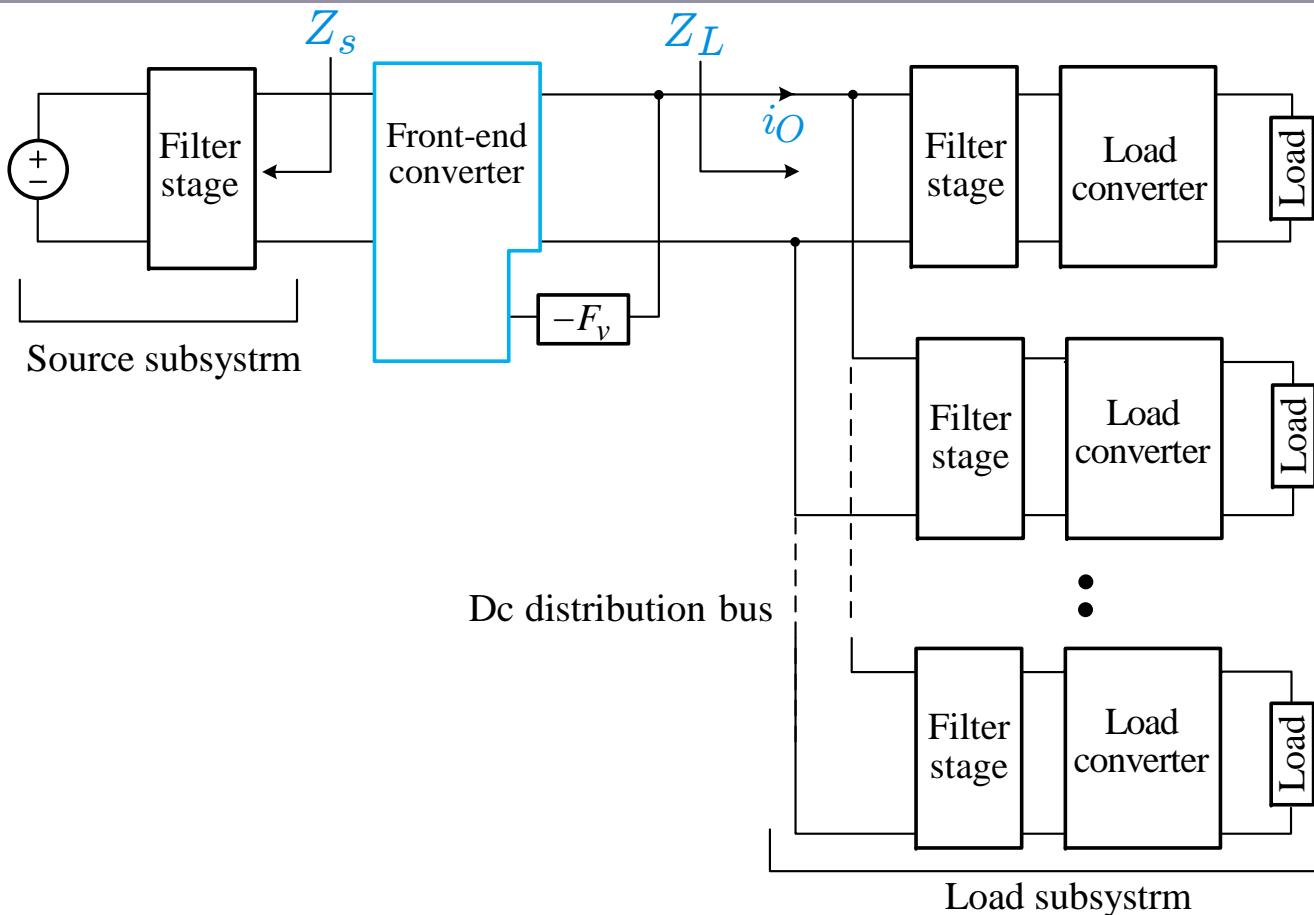
# DC Power Distribution System for Computers



- $Z_s(s)$ : source impedance or output impedance of source subsystem
- $Z_L(s)$ : load impedance or input impedance of load subsystem
- $i_O$ : output current

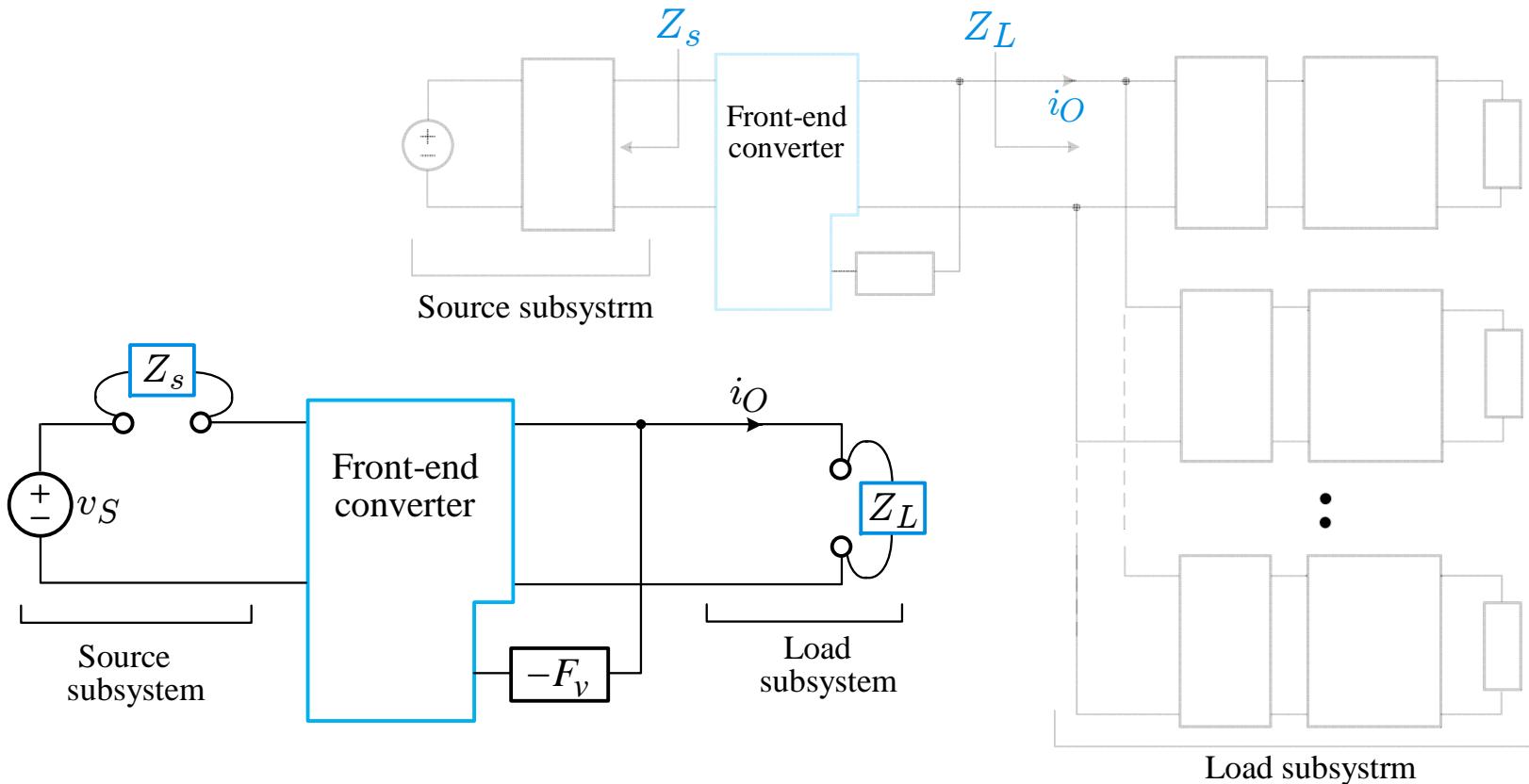
# Equivalent Representation of Front-End Converter




- $v_S$  and  $i_O$  are always known in advance.
- $Z_s(s)$  and  $Z_L(s)$  are unknown or undefined at the design stage of the converter.
- Design should be performed without any knowledge about  $Z_s(s)$  and  $Z_L(s)$ .

# Uncoupled Converter

- Equivalent representation of converter

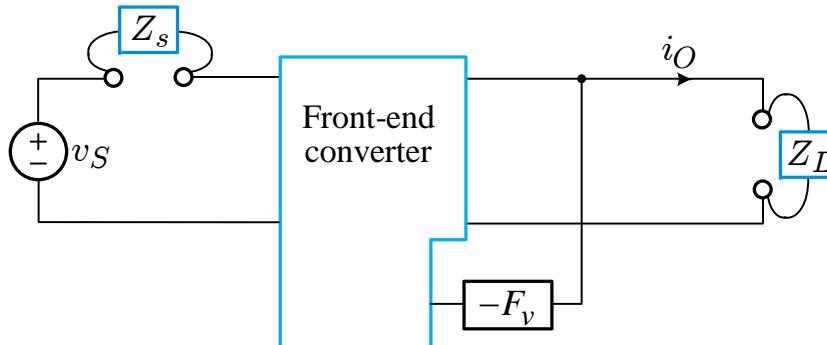

- Uncoupled converter

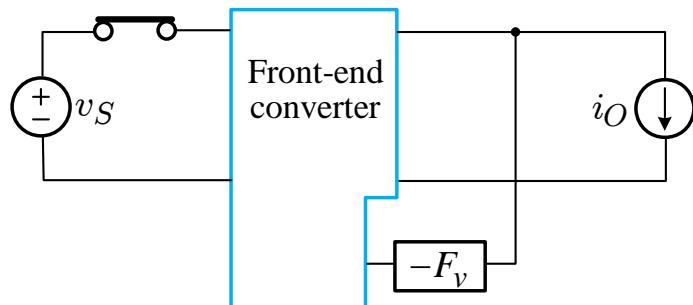


$Z_s(s) = 0$ :  $v_S$  is an ideal voltage source  
 $Z_L(s) = \infty$ :  $i_O$  is an ideal current sink

The control can be designed independently from the unknown  $Z_s(s)$  and  $Z_L(s)$ .


The converter performance can be evaluated with an ideal voltage source and current sink.

Whenever the information about  $Z_s(s)$  and  $Z_L(s)$  is available, the converter performance can be analyzed using the Extra Element Theorem.

# Uncoupled Buck Converter

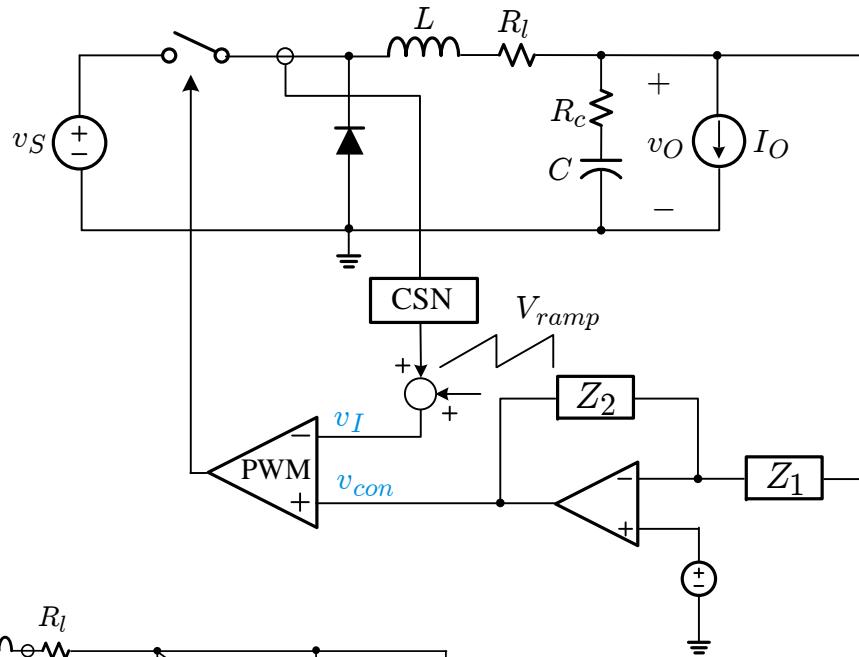


- Small-signal model

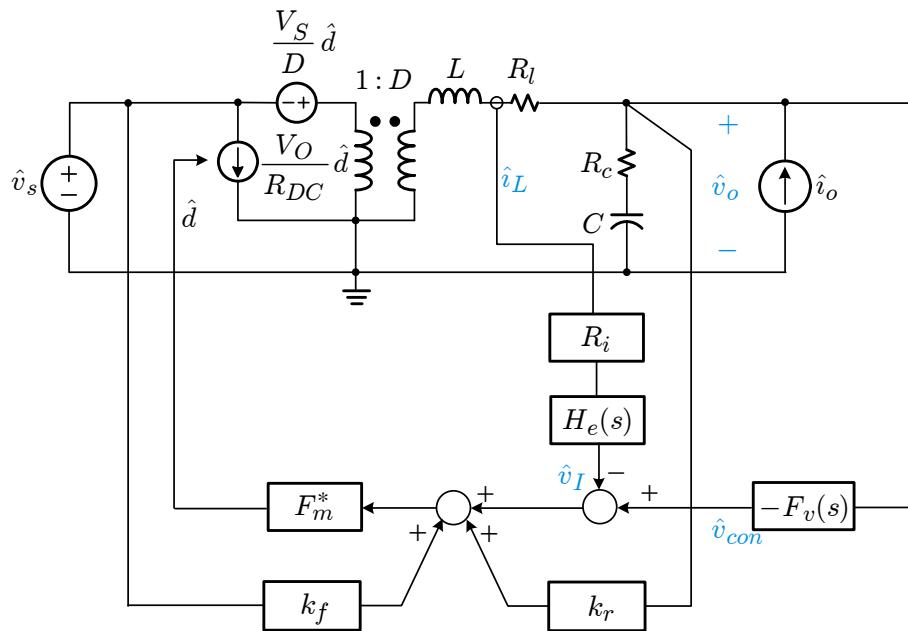

$$R_{DC} = \frac{V_o}{I_o} : \text{DC load parameter}$$

# Control-to-Output Transfer Function

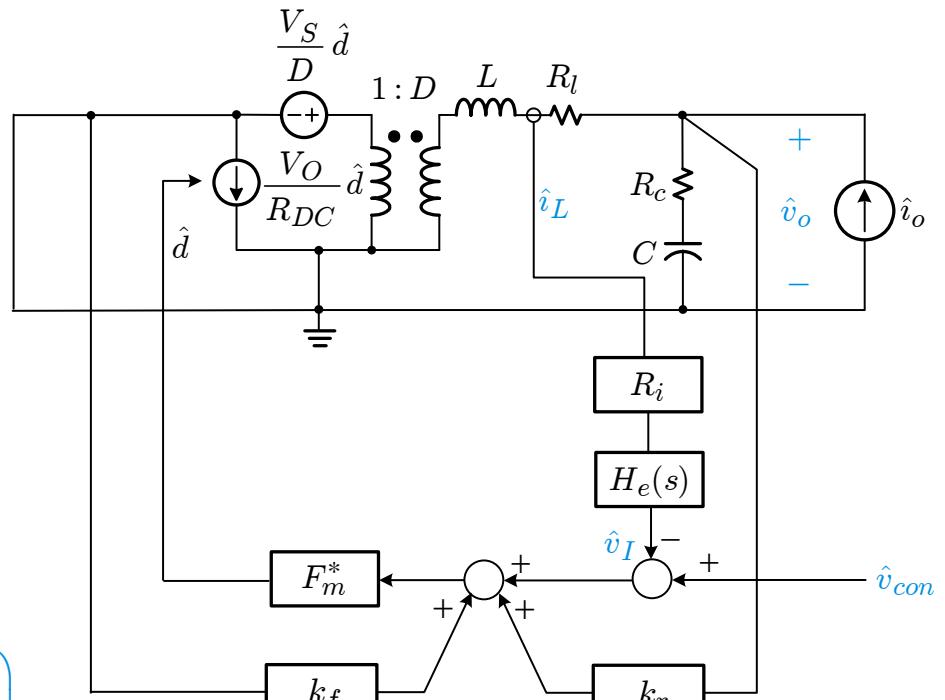

$$\bullet G_{vci}(s) = \frac{\hat{v}_o}{\hat{v}_{con}} \approx K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right) \left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right) \left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$$


$$K_{vc} = \frac{L}{R_i} \frac{1}{T_s(m_c D' - 0.5)} \quad \omega_{pl} = \frac{T_s(m_c D' - 0.5)}{LC} \quad \text{with } m_c = 1 + \frac{S_e}{S_n}$$

Other parameters are the same as the case of a resistive load.

- The DC load parameter  $R_{DC}$  does not appear in the transfer function.
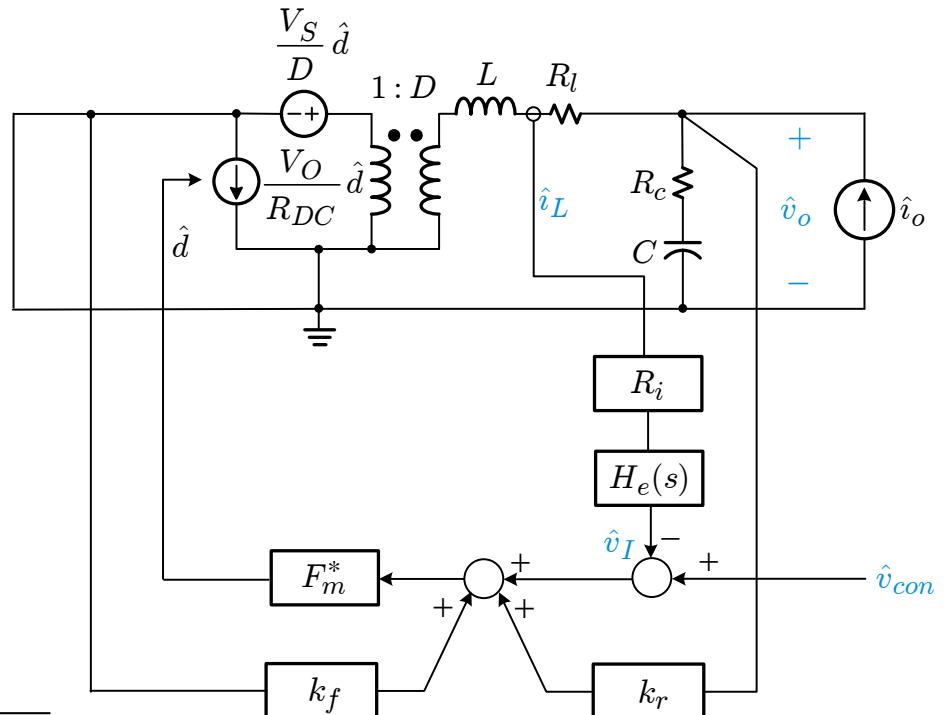
# Current Loop Design


$$G_{vci}(s) = \frac{\hat{v}_o}{\hat{v}_{con}} \approx K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right)\left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right)\left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$$



- Current loop design remains the same as the resistor load case.


$$0.3 < Q_p = \frac{1}{\pi \left( \left( 1 + \frac{S_e}{S_n} \right) D' - 0.5 \right)} < 1.3$$

# Voltage Loop Design

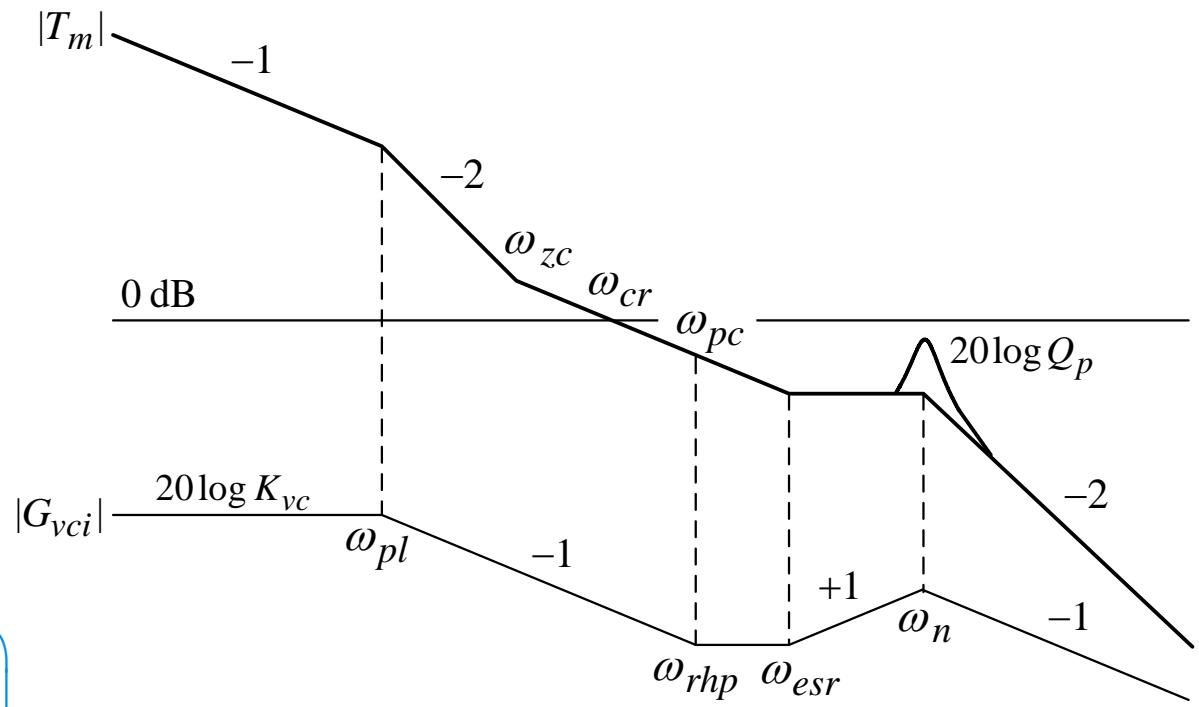

- $$F_v(s) = \frac{K_v \left(1 + \frac{s}{\omega_{zc}}\right)}{s \left(1 + \frac{s}{\omega_{pc}}\right)}$$
- $$T_m(s) = G_{vci}(s) F_v(s) = K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right) \left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right) \left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)} \frac{K_v \left(1 + \frac{s}{\omega_{zc}}\right)}{s \left(1 + \frac{s}{\omega_{pc}}\right)}$$

# Voltage Feedback Compensation

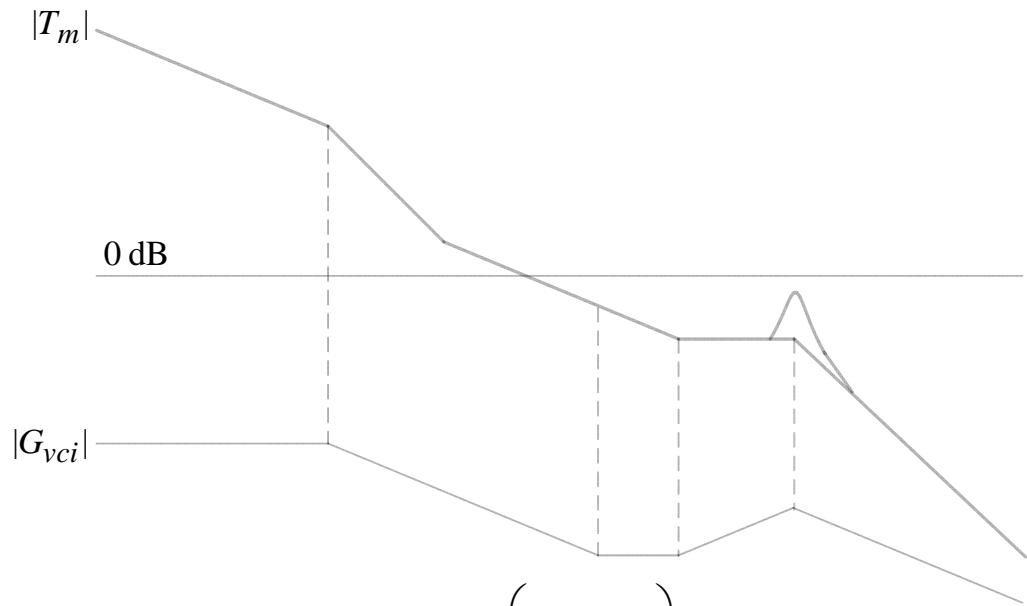


- $$T_m(s) = K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right)\left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right)\left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)} F_v(s) \quad \text{with} \quad F_v(s) = \frac{K_v \left(1 + \frac{s}{\omega_{zc}}\right)}{s \left(1 + \frac{s}{\omega_{pc}}\right)}$$
- Selections of  $F_v(s)$  parameters is the same as the case of a resistive load.
- $$\omega_{pc} = \min \{ \omega_{rhp}, \omega_{esr}, \omega_s / 2 \} \quad \omega_{zc} = (0.6 - 0.8) \omega_o \quad K_v = \frac{\omega_{zc} \omega_{cr}}{K_{vc} \omega_{pl}}$$
- Voltage loop design becomes the same provided that the product  $K_{vc} \omega_{pl}$  remains unchanged.


# $K_{vc} \omega_{pl}$ Product Comparison

$G_{vci}(s) \approx K_{vs} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right)\left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right)\left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$		
	Uncoupled converter	Converter with resistive load
$K_{vc}$	$\frac{L}{R_i} \frac{1}{T_s(m_c D' - 0.5)}$	$\frac{R}{R_i} \frac{1}{1 + \frac{RT_s}{L} (m_c D' - 0.5)}$
$\omega_{pl}$	$\frac{T_s(m_c D' - 0.5)}{LC}$	$\frac{1}{CR} \left(1 + \frac{RT_s}{L} (m_c D' - 0.5)\right)$
$K_{vc} \omega_{pl}$	$\frac{1}{R_i C}$	$\frac{1}{R_i C}$

# Control Design Summary

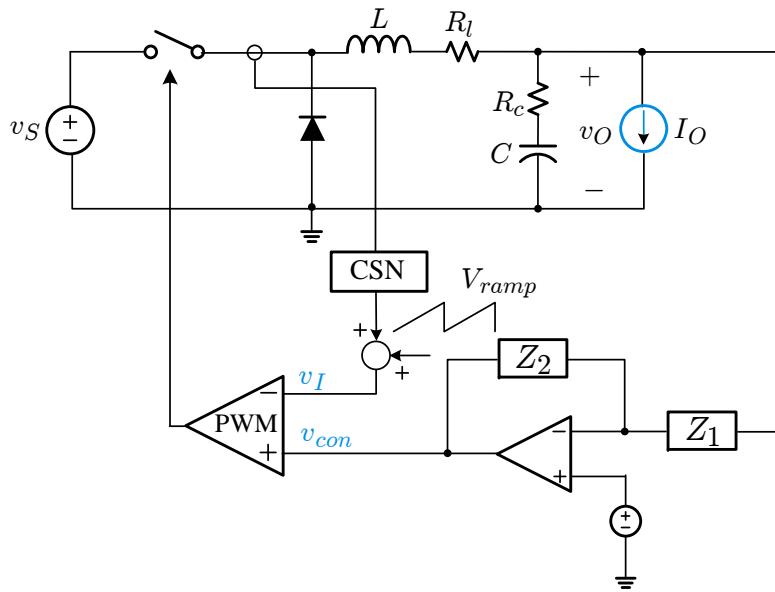

Uncoupled buck converter

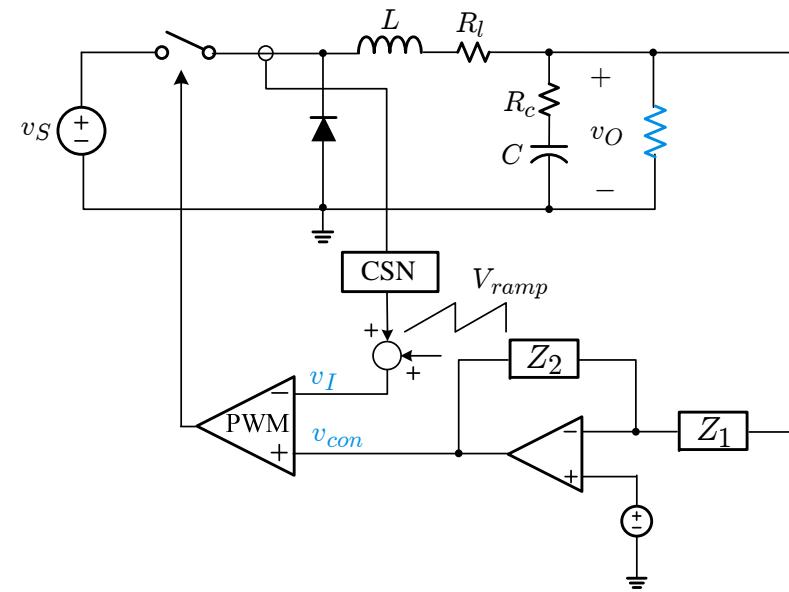


Resistor-coupled buck converter


- Control design of the uncoupled converter remains the same as the resistor-loaded converter.
- Standard design procedures for resistive loads are adoptable to uncoupled converters.
- Conclusions can be extended to other onverter topologies.

# Converter Performance


Loop gain

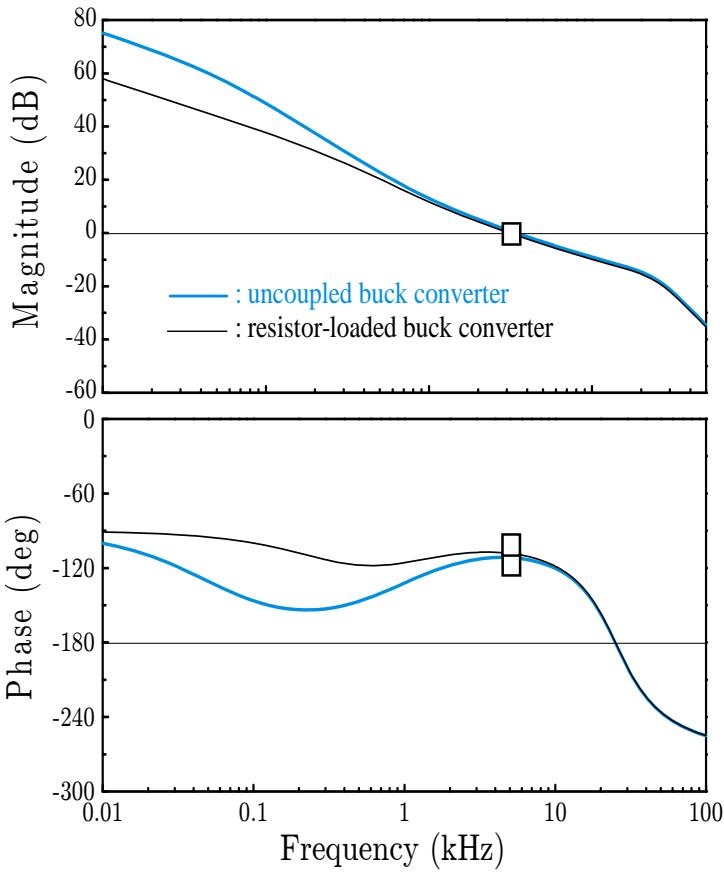

Output impedance


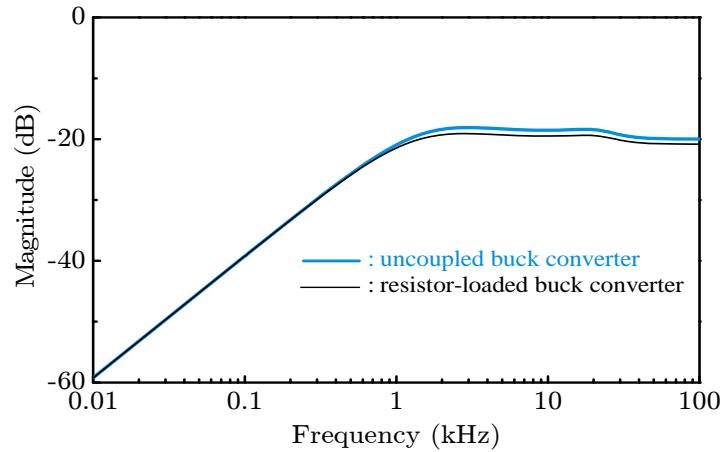


Audio-susceptibility

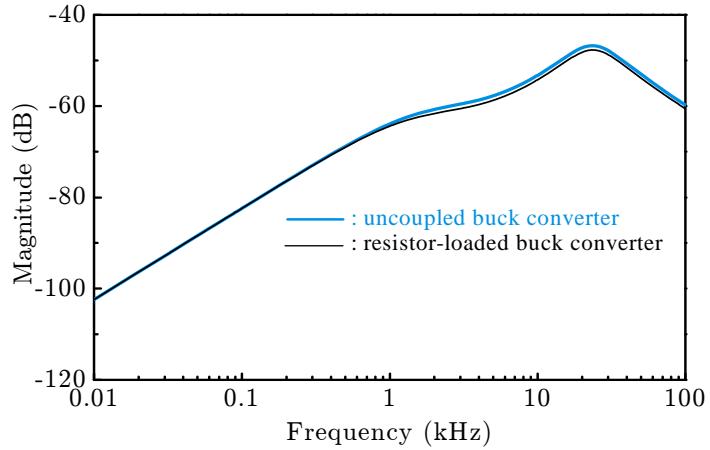


# Uncoupled Boost Converter

- Small-signal model

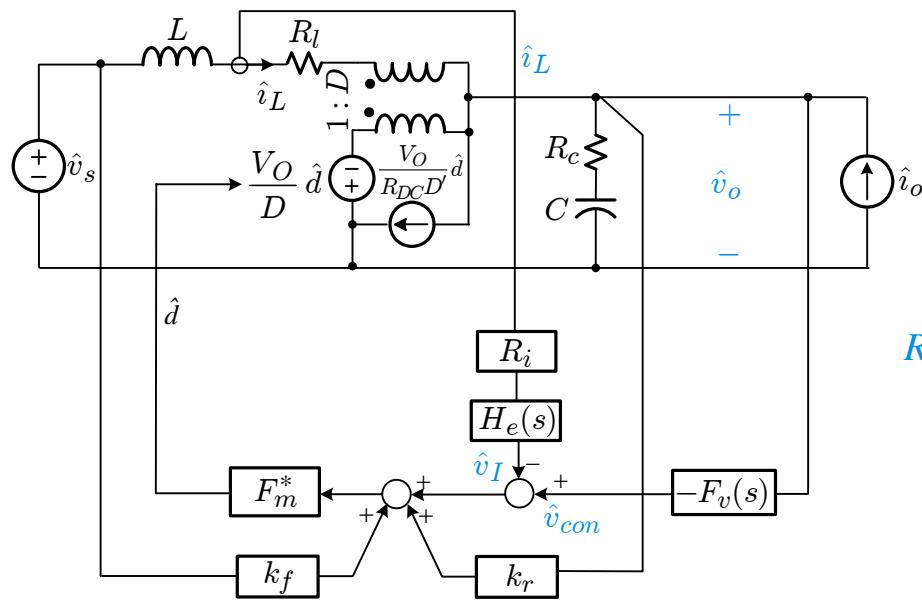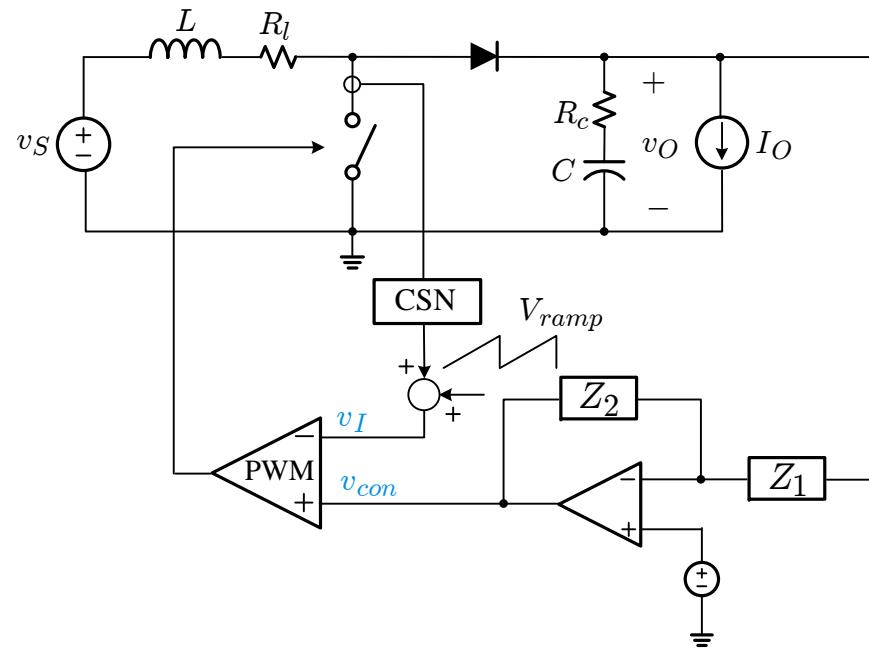

$$R_{DC} = \frac{V_O}{I_O} : \text{DC load parameter}$$

# Control-to-Output Transfer Function

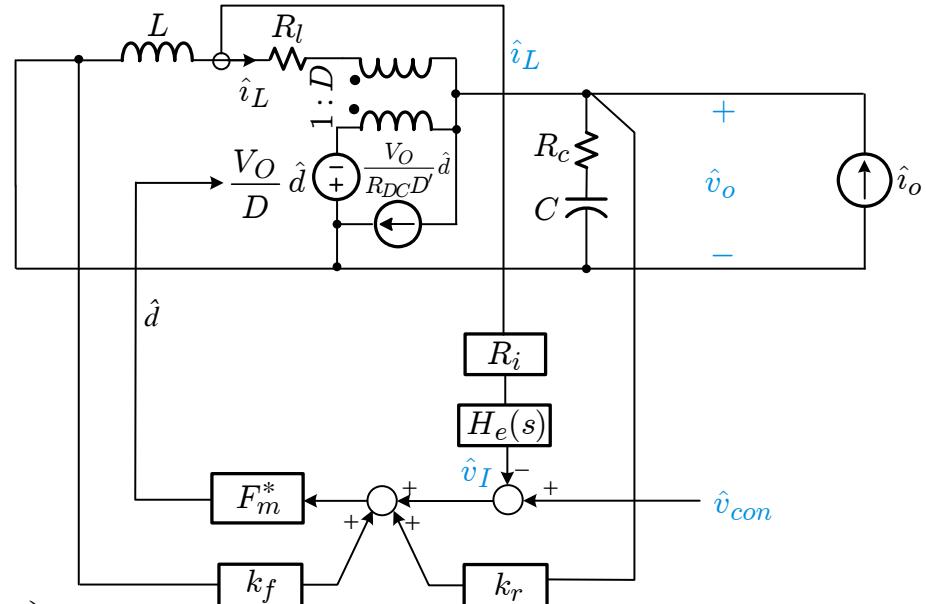

- $$G_{vci}(s) = \frac{\hat{v}_o}{\hat{v}_{con}} \approx K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right) \left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right) \left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$$

$$K_{vc} = \frac{L}{R_i} \frac{1}{T_s D'^2 (m_c D' - 0.5) + \frac{L}{R_{DC} D'}}$$

$$\omega_{pl} = \frac{T_s D'^2 (m_c D' - 0.5) + \frac{L}{R_{DC} D'}}{\frac{LC}{D'}} \quad \omega_{rhp} = \frac{R_{DC} D'^2}{L}$$


- The DC load parameter  $R_{DC}$  is a key parameter.

# $K_{vc} \omega_{pl}$ Product Comparison


$G_{vci}(s) \approx K_{vs} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right)\left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right)\left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$		
	Uncoupled converter	Converter with resistive load
$K_{vc}$	$\frac{L}{R_i} \frac{1}{T_s D'^2 (m_c - 0.5) + \frac{L}{R_{DC} D'}}$	$\frac{L}{R_i} \frac{1}{T_s D'^2 (m_c - 0.5) + \frac{2L}{RD'}}$
$\omega_{pl}$	$\frac{T_s D'^2 (m_c - 0.5) + \frac{L}{R_{DC} D'}}{\frac{LC}{D'}}$	$\frac{T_s D'^2 (m_c - 0.5) + \frac{2L}{RD'}}{\frac{LC}{D'}}$
$K_{vc} \omega_{pl}$	$\frac{D'}{R_i C}$	$\frac{D'}{R_i C}$

# Converter Performance

Loop gain

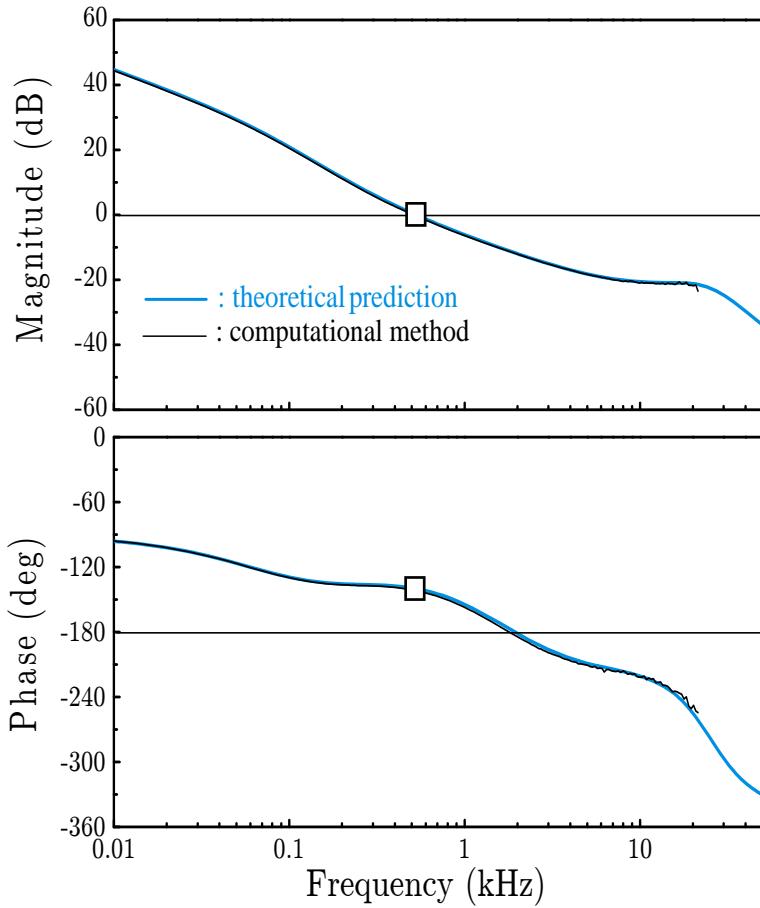


Output impedance

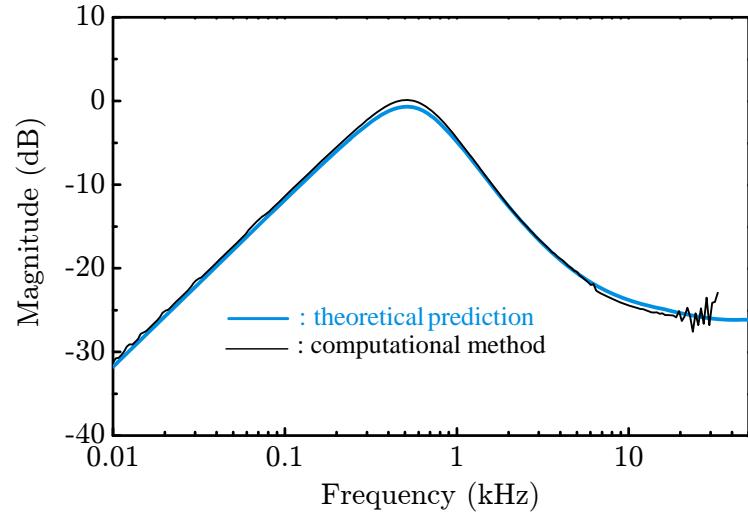

# Buck/Boost Converter

$G_{vci}(s) \approx K_{vs} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right)\left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right)\left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$		
	Uncoupled converter	Converter with resistive load
$K_{vc}$	$\frac{L}{R_i} \frac{1}{T_s D'^2 (m_c - 0.5) + \frac{DL}{R_{DC} D'}}$	$\frac{L}{R_i} \frac{1}{T_s D'^2 (m_c - 0.5) + \frac{(1+D)L}{RD'}}$
$\omega_{pl}$	$\frac{T_s D'^2 (m_c - 0.5) + \frac{DL}{R_{DC} D'}}{\frac{LC}{D'}}$	$\frac{T_s D'^2 (m_c - 0.5) + \frac{(1+D)L}{RD'}}{\frac{LC}{D'}}$
$K_{vc} \omega_{pl}$	$\frac{D'}{R_i C}$	$\frac{D'}{R_i C}$

# Middlebrook's Extra Element Theorem

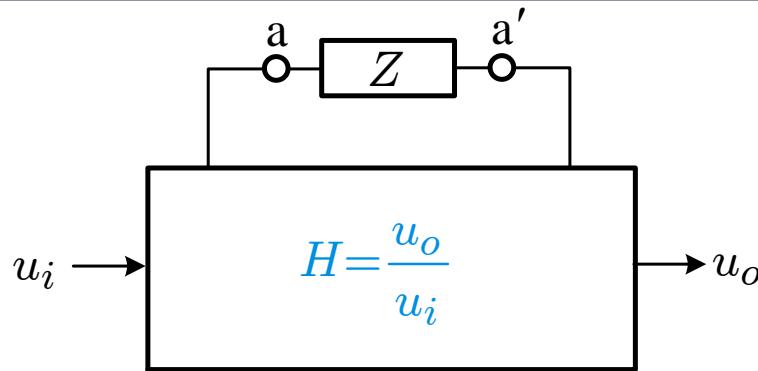

- Definitions

$H(s) = \frac{u_o(s)}{u_i(s)}$ : transfer gain of interest

$Z(s)$ : impedance of the circuit component which is designated as **the extra element**


$$\bullet \text{ The Extra Element Theorem: } H(s) = H_\infty(s) \frac{1 + \frac{\bar{\zeta}(s)}{Z(s)}}{1 + \frac{\bar{z}(s)}{Z(s)}}$$

$H_\infty(s)$ : transfer gain  $H(s)$  evaluated with the extra element removed, denoted as the open-circuit transfer gain


$\bar{z}(s)$ : input impedance looking into a-a' with the input variable  $u_i(s)$  disabled, denoted as the driving point impedance

$\bar{\zeta}(s)$ : input impedance looking into a-a' with the input variable  $u_o(s)$  nullified, denoted as the null driving point impedance


# Pictorial Illumination

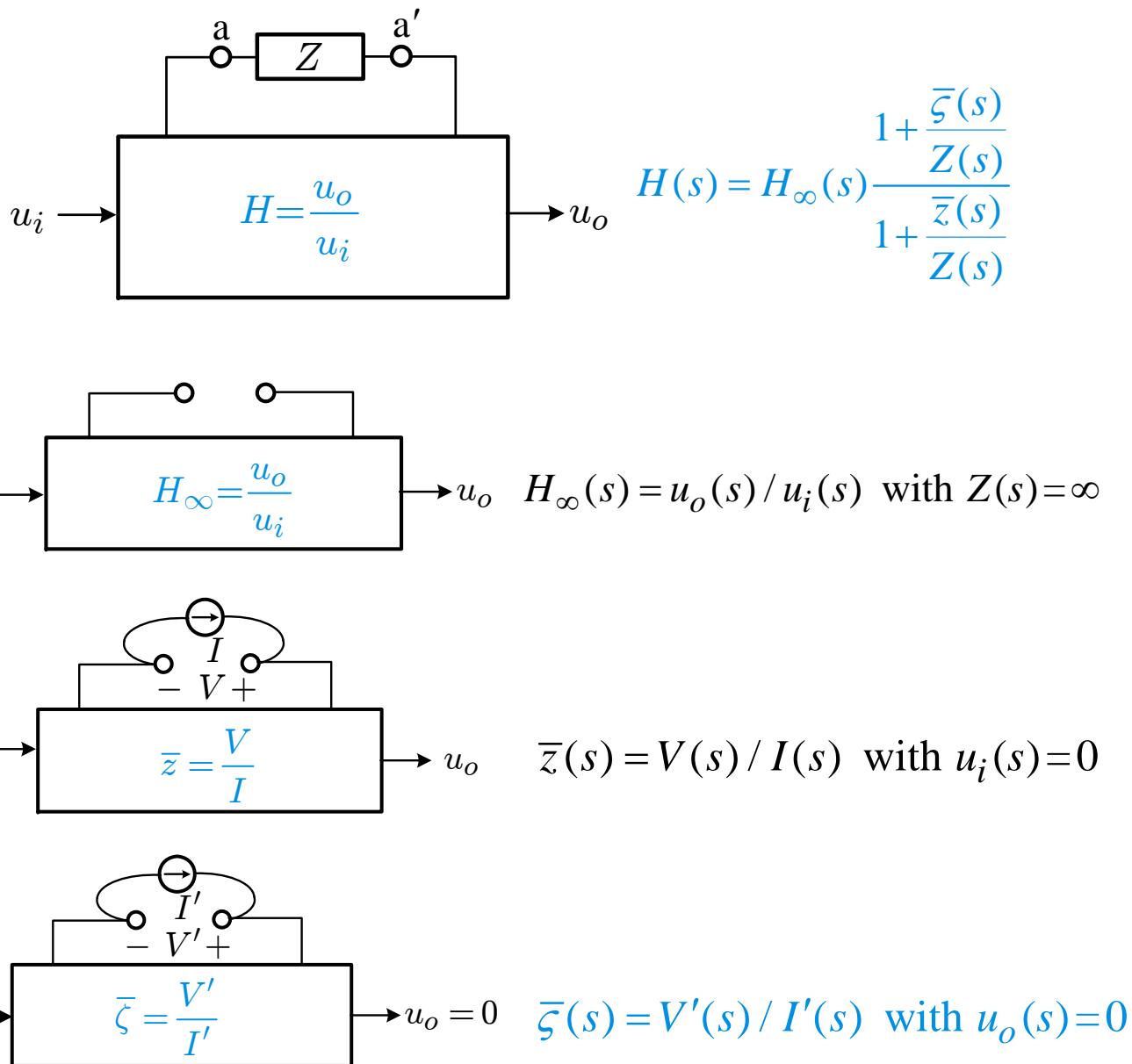

# Application to MOSFET Amplifier

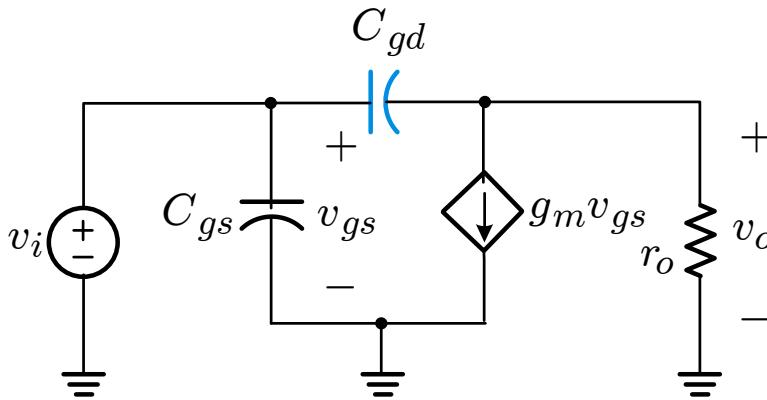

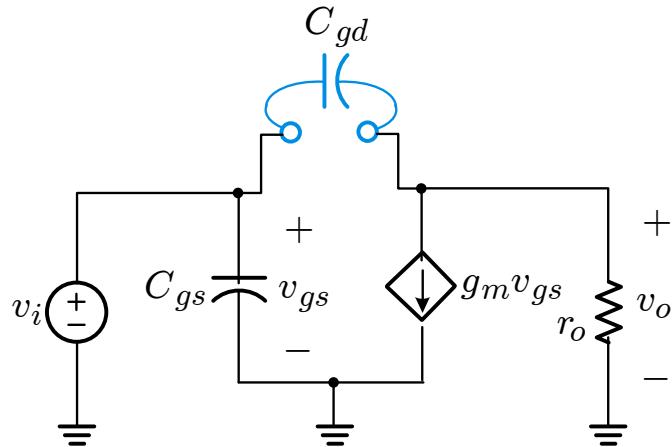- Evaluate the voltage gain  $\frac{v_o(s)}{v_i(s)}$  using EET
- Consider  $C_{gd}$  as the extra element




$$H(s) = \frac{v_o(s)}{v_i(s)} = H_\infty(s) \frac{1 + \frac{\bar{\zeta}(s)}{Z(s)}}{1 + \frac{\bar{z}(s)}{Z(s)}}$$


$$\text{with } Z(s) = \frac{1}{sC_{gd}}$$
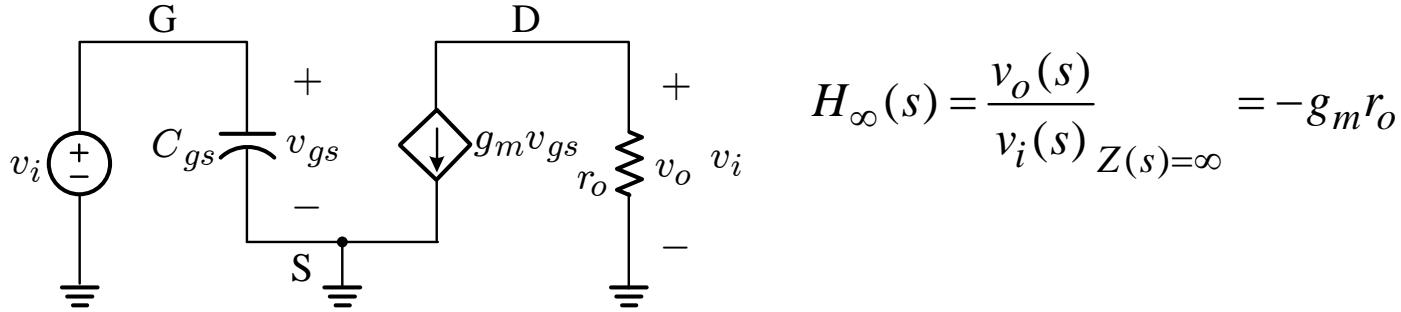
# Application to MOSFET Amplifier

- MOSFET amplifier with  $C_{gd} = 0 \Rightarrow Z(s) = \frac{1}{sC_{gd}} = \infty$




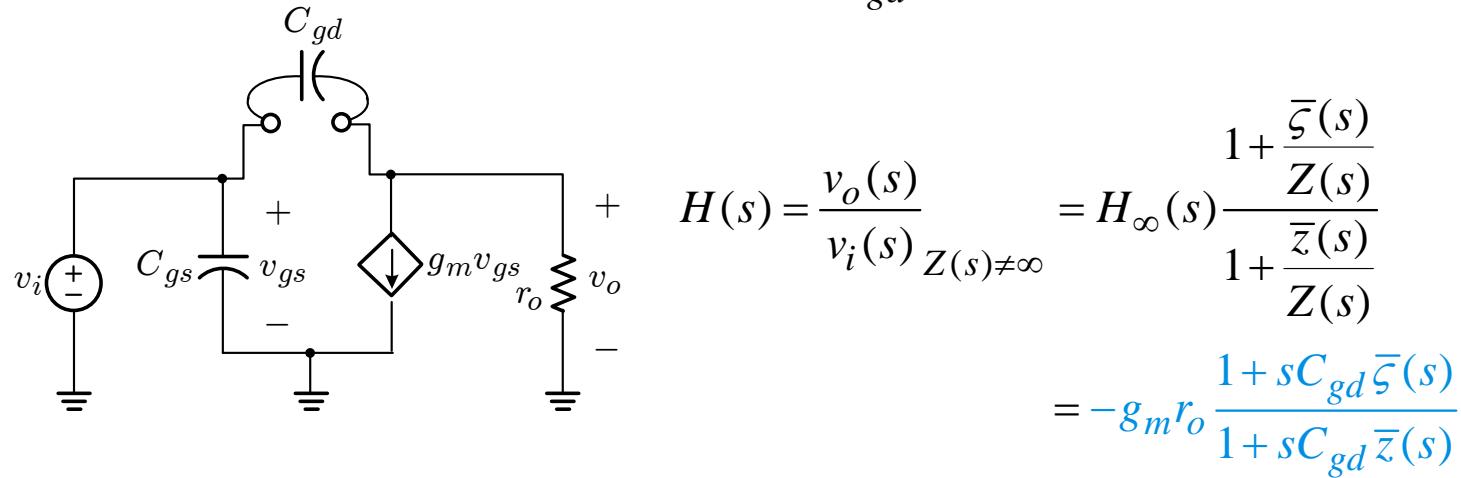- MOSFET amplifier with  $C_{gd} \neq 0 \Rightarrow Z(s) = \frac{1}{sC_{gd}} \neq \infty$




# Application to MOSFET Amplifier

- Evaluation of  $\bar{z}(s)$

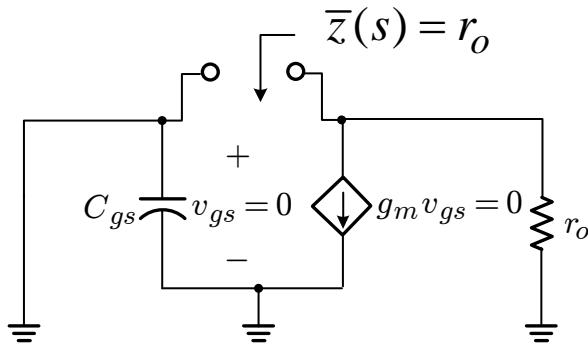

- Evaluation of  $\bar{\zeta}(s) = \frac{v_T(s)}{i_T(s)} \Big|_{v_o(s)=0}$

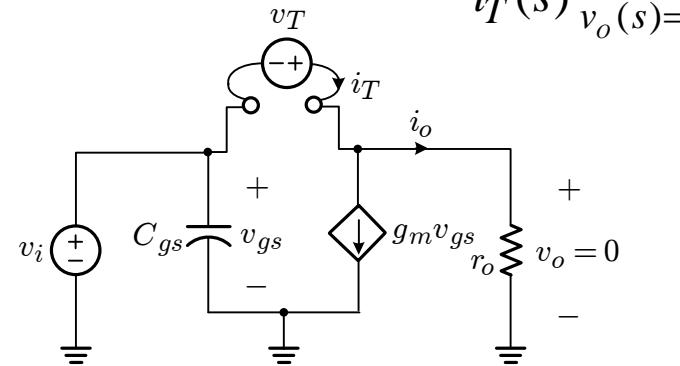


- $v_o(s) = 0 \Rightarrow i_o = 0 \Rightarrow i_T = g_m v_{gs}$
- $v_o(s) = 0 \Rightarrow v_T = -v_{gs}$

$$\bar{\zeta}(s) = \frac{v_T}{i_T} = \frac{-v_{gs}}{g_m v_{gs}} = -\frac{1}{g_m}$$


- Transfer gain  $H(s) = \frac{v_o(s)}{v_i(s)} \Big|_{Z(s) \neq \infty} = -g_m r_o \frac{1 + s C_{gd} \bar{\zeta}(s)}{1 + s C_{gd} \bar{z}(s)}$

$$= -g_m r_o \frac{s C_{gd}}{1 + s C_{gd} r_o}$$


# Alternative Form of EET

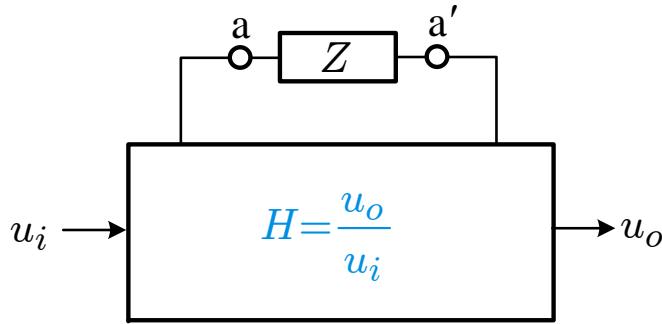

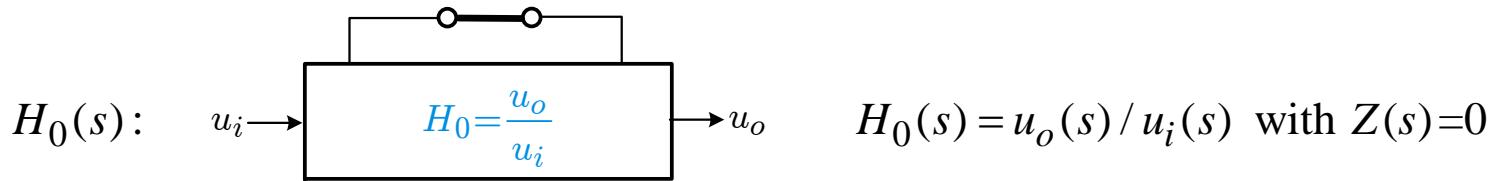
$$H(s) = H_0(s) \frac{1 + \frac{Z(s)}{\bar{\zeta}(s)}}{1 + \frac{Z(s)}{\bar{z}(s)}}$$


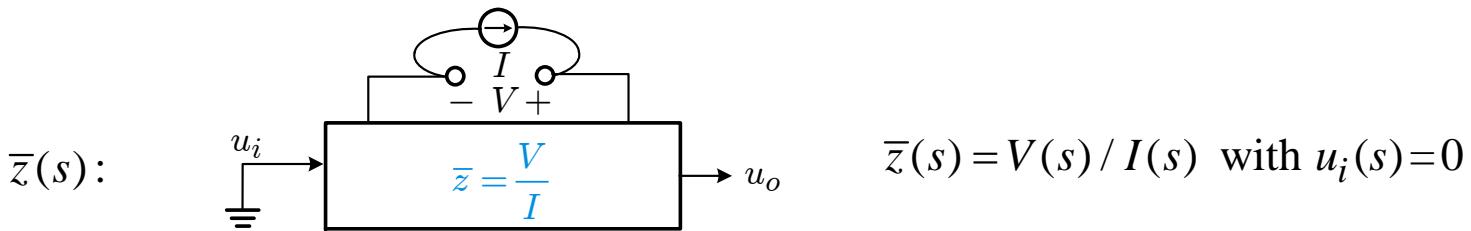
$$H_0(s) = u_o(s) / u_i(s) \text{ with } Z(s)=0$$



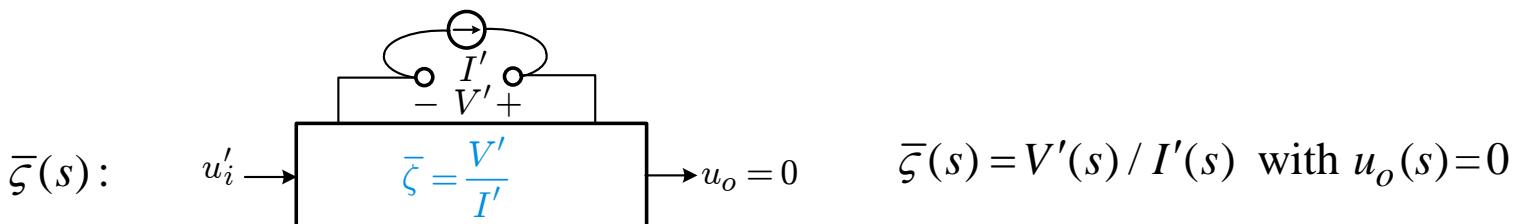
$$\bar{z}(s) = V(s) / I(s) \text{ with } u_i(s)=0$$




$$\bar{\zeta}(s) = V'(s) / I'(s) \text{ with } u_o(s)=0$$


# Extension to 2 EET

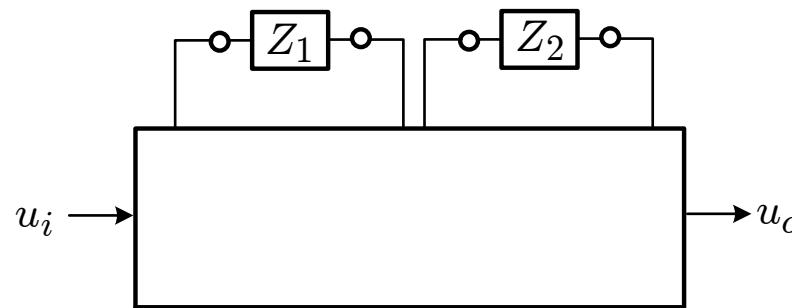

- First adoption of EET

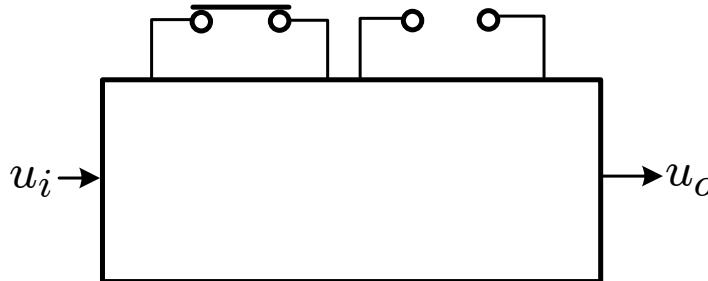


$$\frac{u_o(s)}{u_i(s)} \Big|_{Z_1(s)=0, Z_2(s)=\infty} = H_s(s)$$


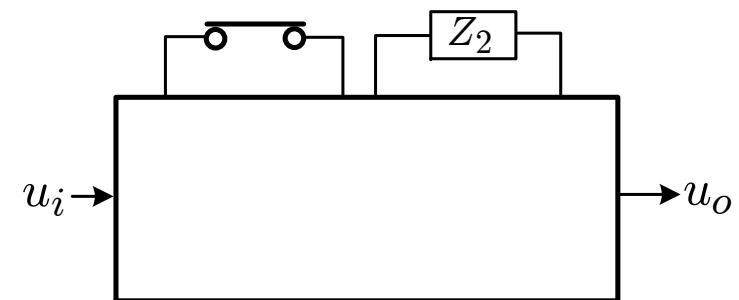


$$\frac{u_o(s)}{u_i(s)} \Big|_{\substack{Z_1(s)=0 \\ Z_2(s) \neq \infty}} = H_s(s) \frac{\frac{1 + \bar{\zeta}_2(s)}{Z_2(s)}}{1 + \frac{\bar{z}_2(s)}{Z_2(s)}}$$

# Extension of EET- 2 EET

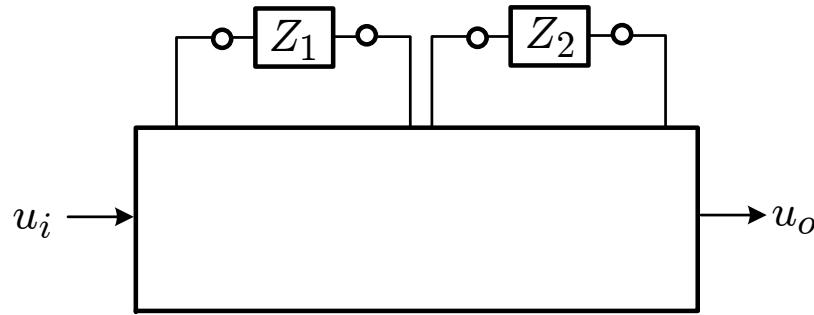

- Second adoption of EET

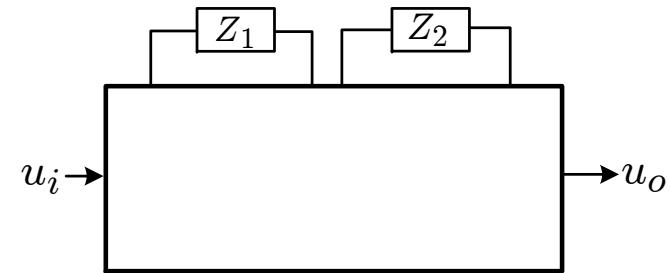
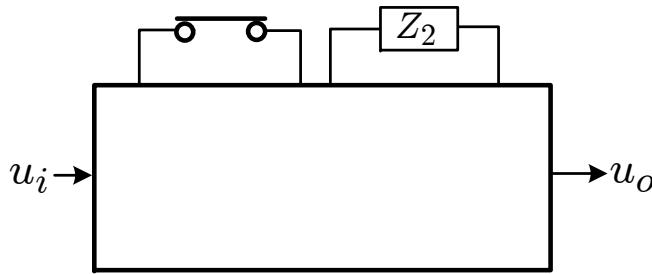


$$\frac{u_o(s)}{u_i(s) \begin{matrix} Z_1(s)=0 \\ Z_2(s)\neq\infty \end{matrix}} = H_s(s) \frac{1 + \frac{\bar{\zeta}_2(s)}{Z_2(s)}}{1 + \frac{\bar{z}_2(s)}{Z_2(s)}}$$



$$\frac{u_o(s)}{u_i(s) \begin{matrix} Z_1(s)\neq 0 \\ Z_2(s)\neq\infty \end{matrix}} = \left( \begin{array}{c} 1 + \frac{\bar{\zeta}_2(s)}{Z_2(s)} \\ H_s(s) \frac{1 + \frac{\bar{\zeta}_1(s)}{Z_1(s)}}{1 + \frac{\bar{z}_1(s)}{Z_1(s)}} \end{array} \right) \left( \begin{array}{c} 1 + \frac{Z_1(s)}{\bar{\zeta}_1(s)} \\ 1 + \frac{Z_2(s)}{\bar{z}_1(s)} \end{array} \right)$$

# Load-Coupled Converter


- Uncoupled converter

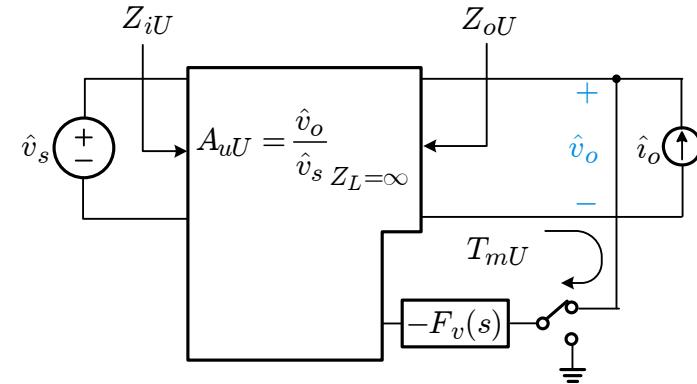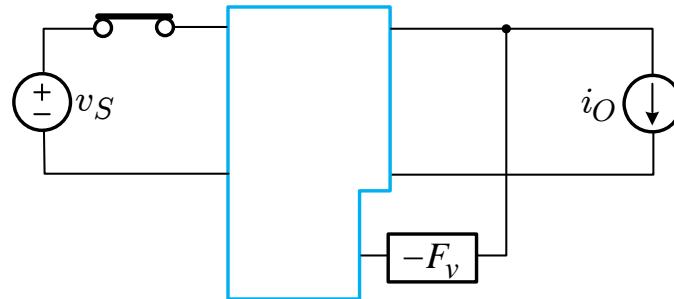

- Load-coupled converter

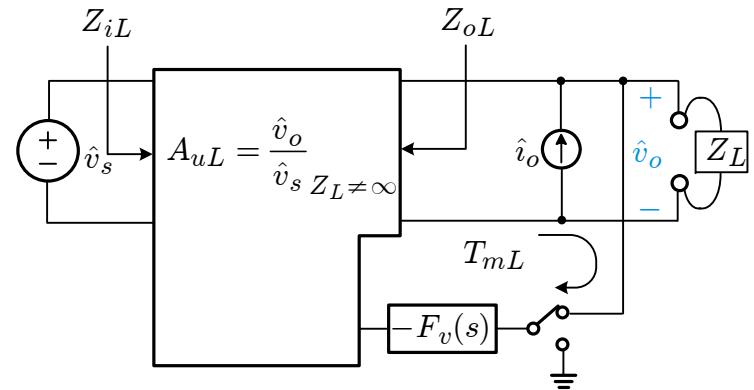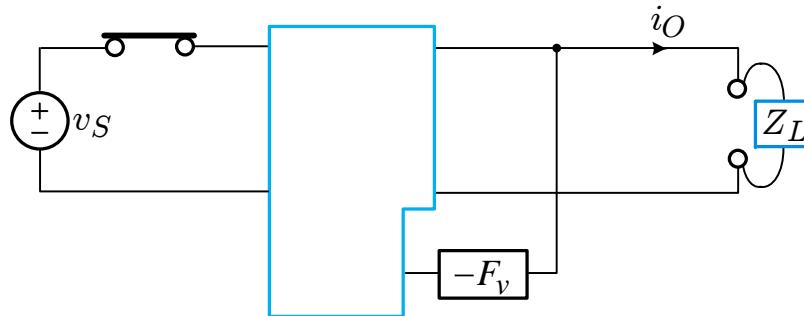

# Performance of Load-Coupled Converter

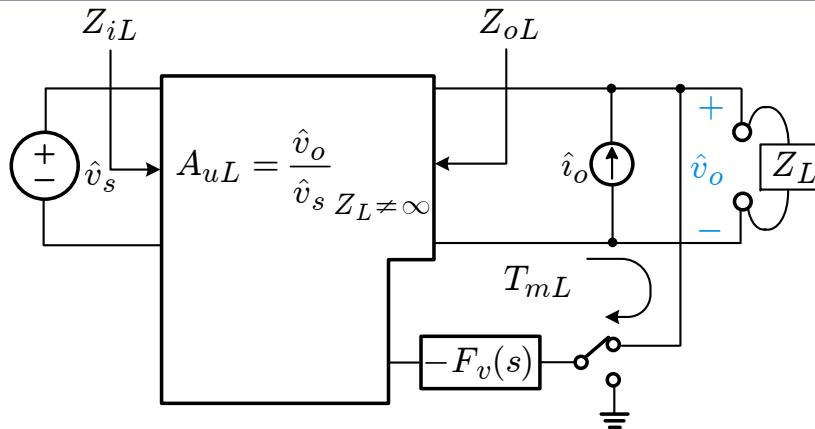


$$A_{uL}(s) = A_{uU}(s) \frac{1}{1 + \frac{Z_{oU}(s)}{Z_L(s)}}$$


$$Z_{oL}(s) = Z_{oU}(s) \frac{1}{1 + \frac{Z_{oU}(s)}{Z_L(s)}}$$

$$T_{mL}(s) = T_{mU}(s) \frac{1}{1 + (1 + T_{mU}(s)) \frac{Z_{oU}(s)}{Z_L(s)}}$$

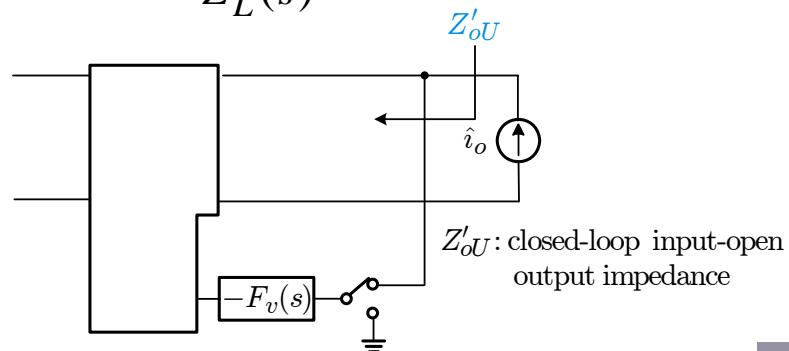
$$Z_{iL}(s) = Z_{iU}(s) \frac{\frac{Z_{oU}(s)}{Z_L(s)}}{1 + \frac{Z'_{oU}(s)}{Z_L(s)}}$$






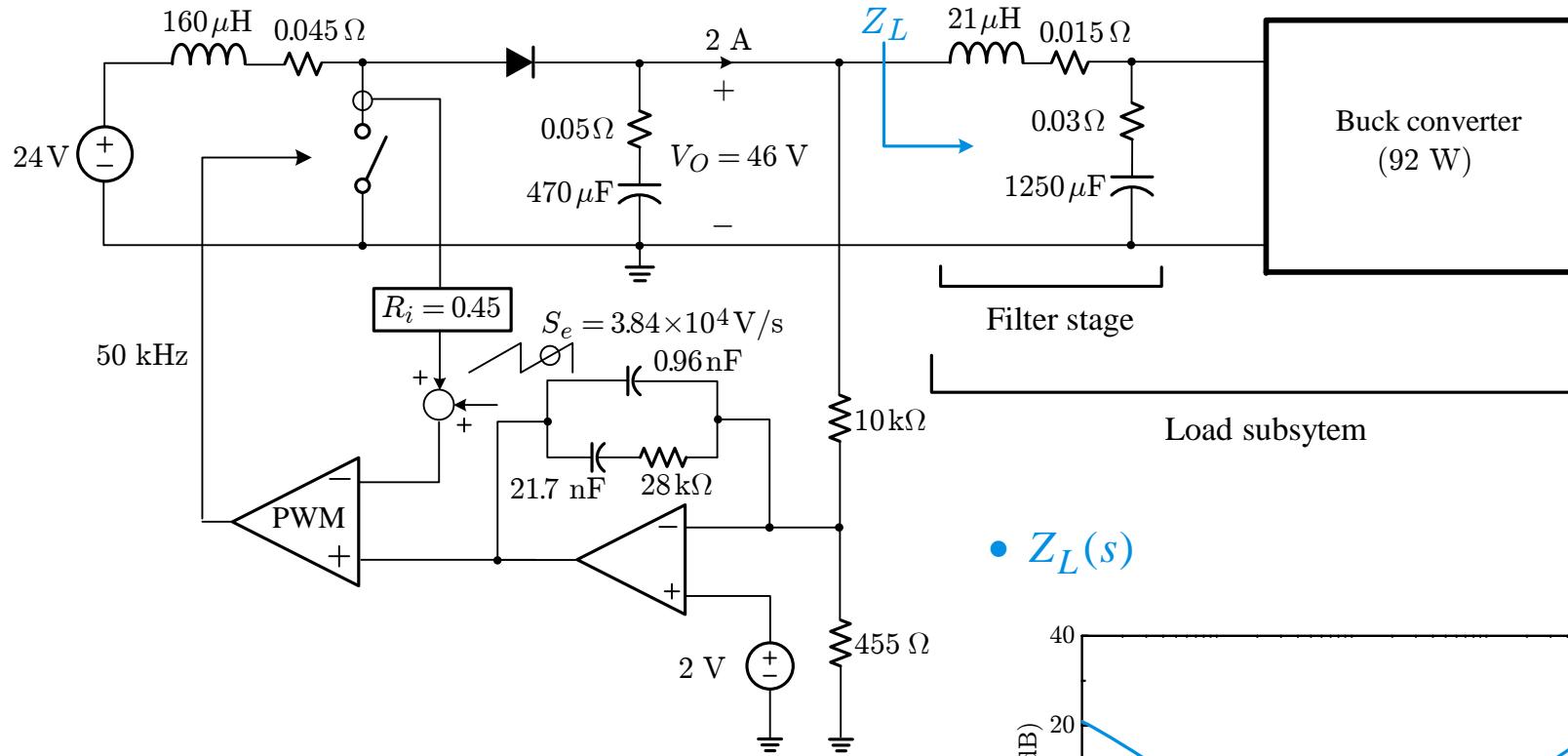
# Performance of Load-Coupled Boost Converter



- $Z_L(s)$

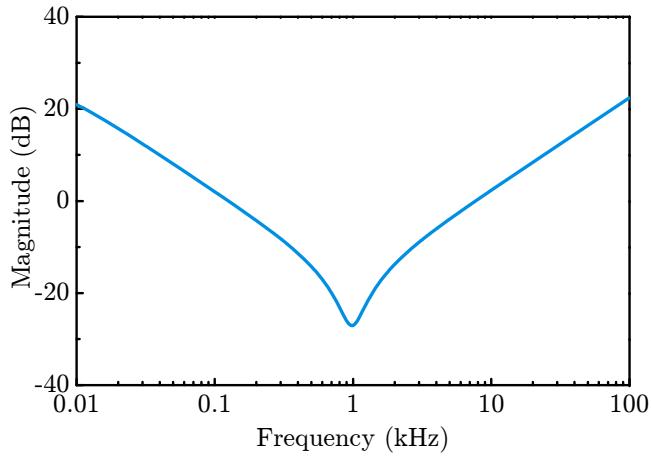

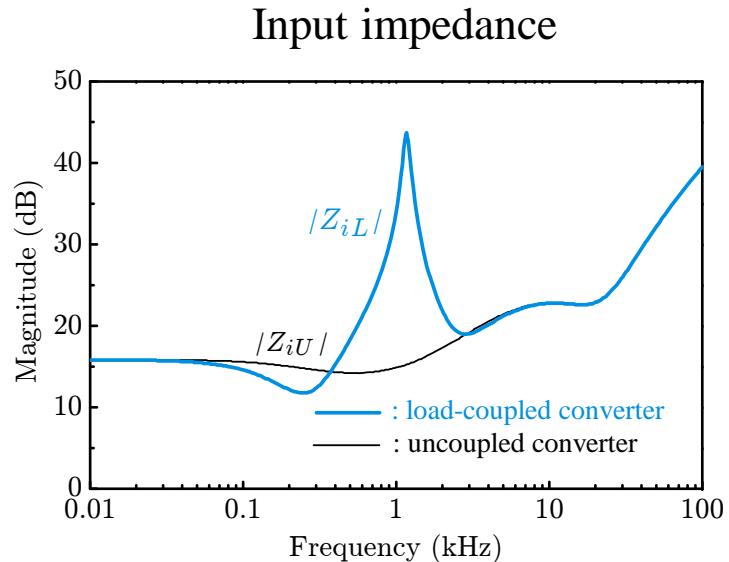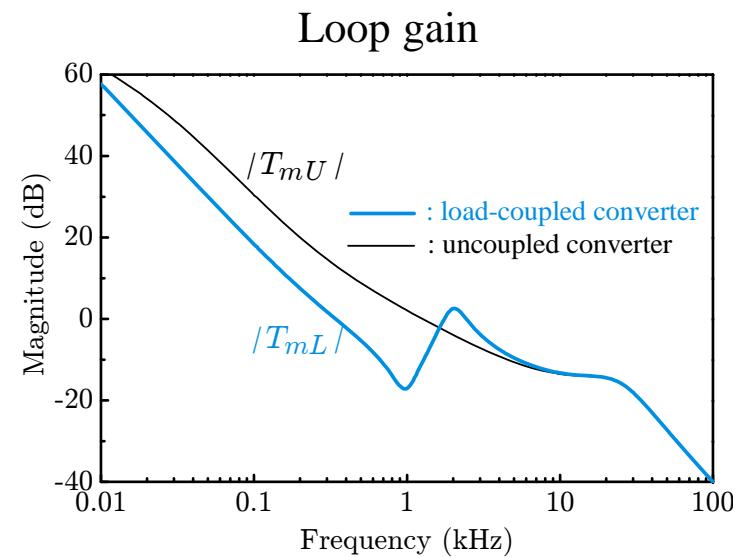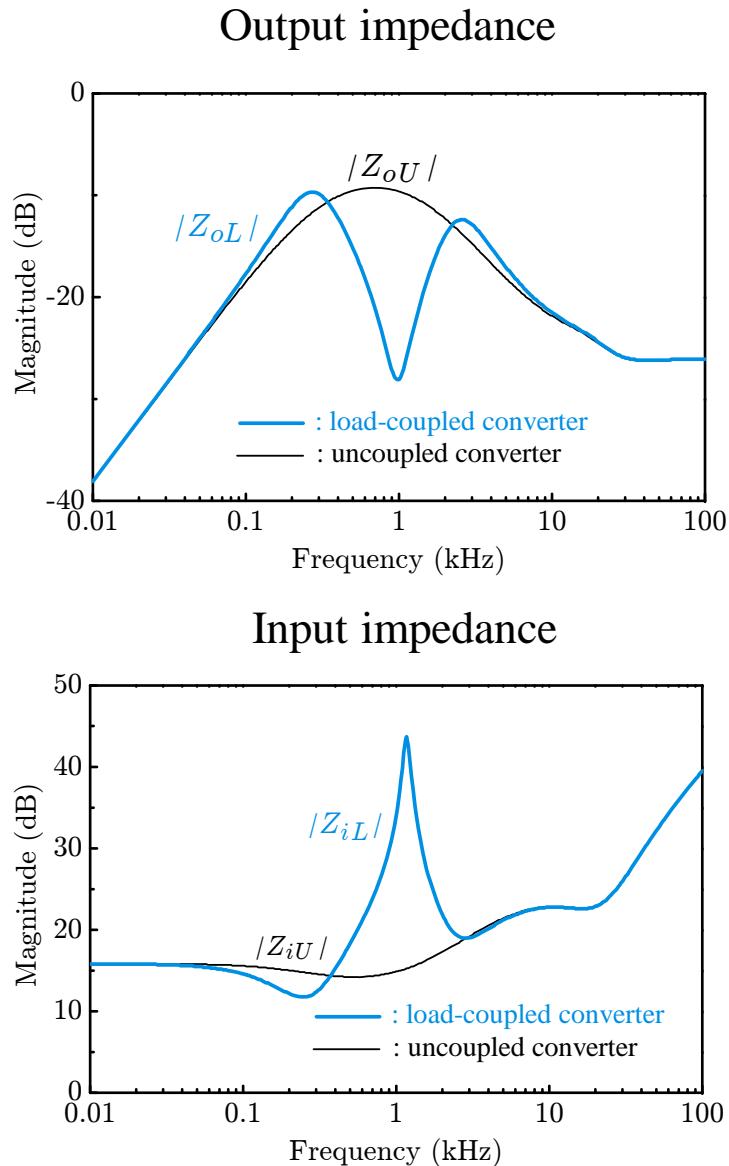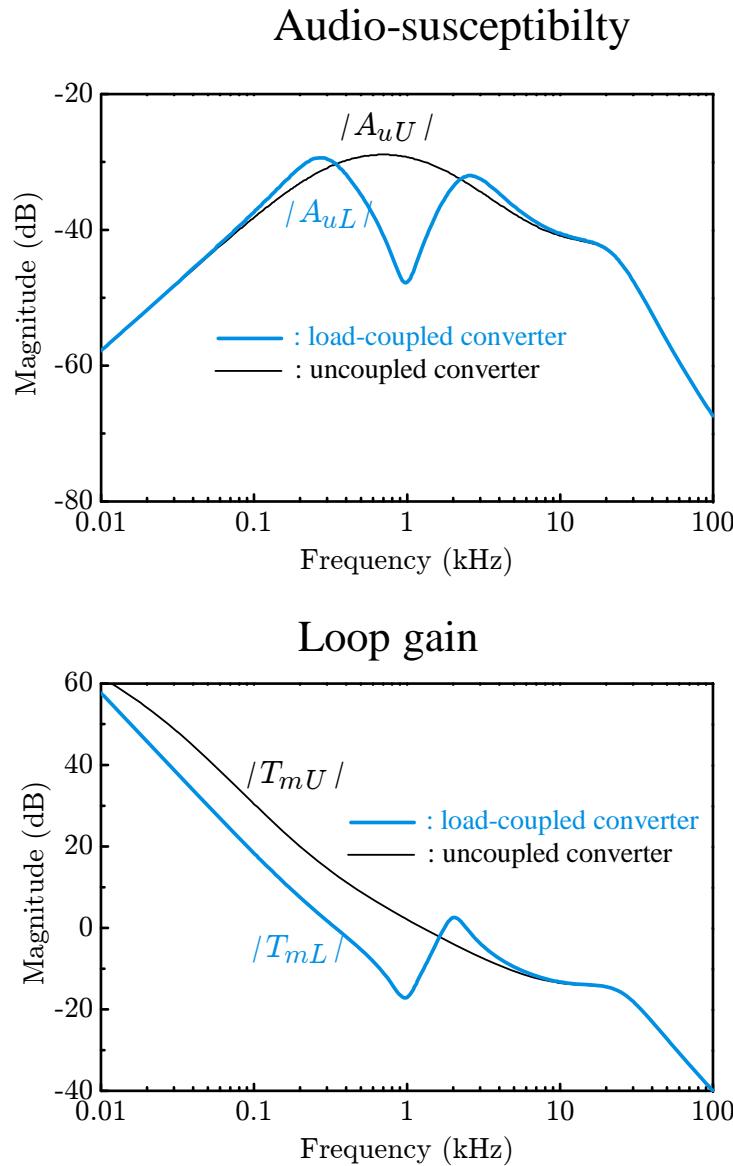
# Performance of Load-Coupled Boost Converter




# Source-Coupled Converter


- Uncoupled converter

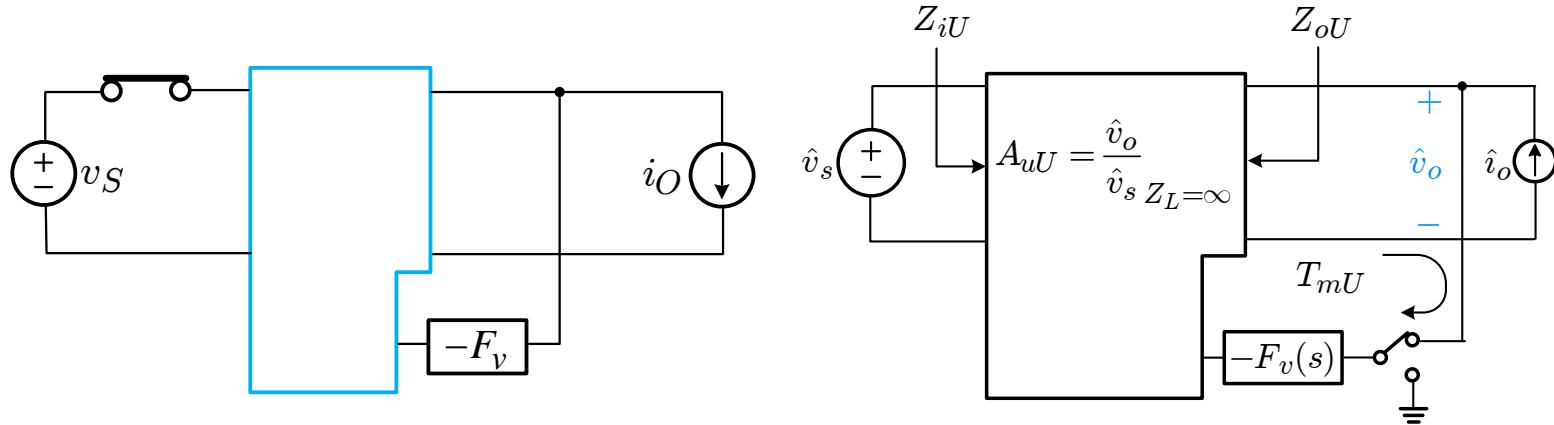

- Source-coupled converter

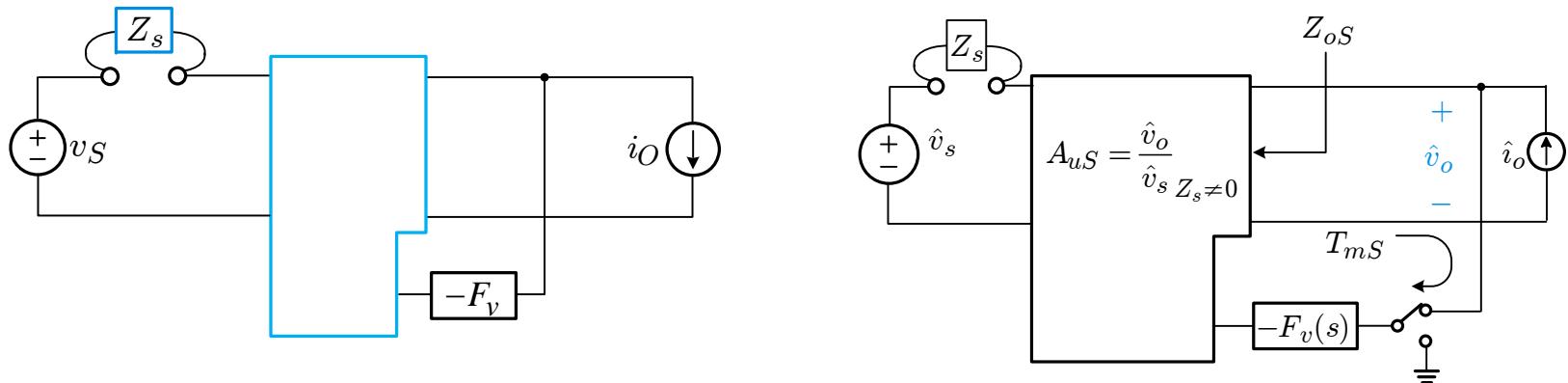
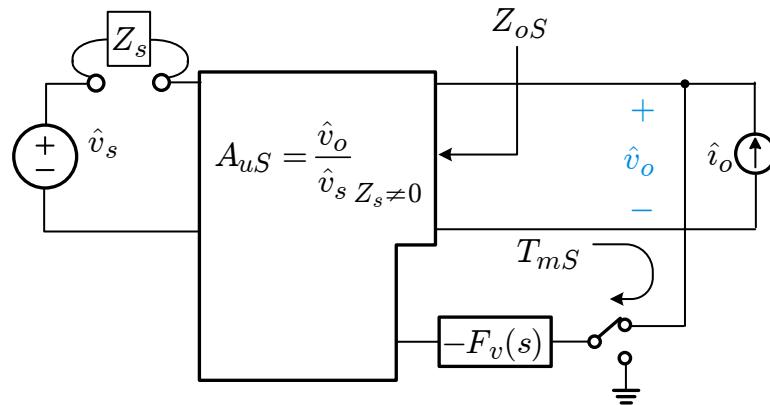
# Performance of Source-Coupled Converter




$$A_{uS}(s) = A_{uU}(s) \frac{1}{1 + \frac{Z_s(s)}{Z_{iU}(s)}}$$


$$Z_{oS}(s) = Z_{oU}(s) \frac{1 + \frac{Z_s(s)}{Z'_i(s)}}{1 + \frac{Z_s(s)}{Z_{iU}(s)}}$$

$$T_{mS}(s) = T_{mU}(s) \frac{1 + \frac{Z_s(s)}{Z''_i(s)}}{1 + \frac{Z_s(s)}{Z'''_i(s)}}$$


# Input Impedance Definition

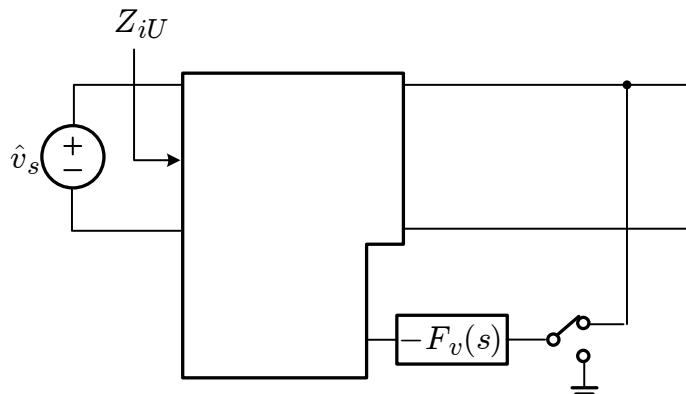


$Z_{iU}$ : closed-loop input impedance

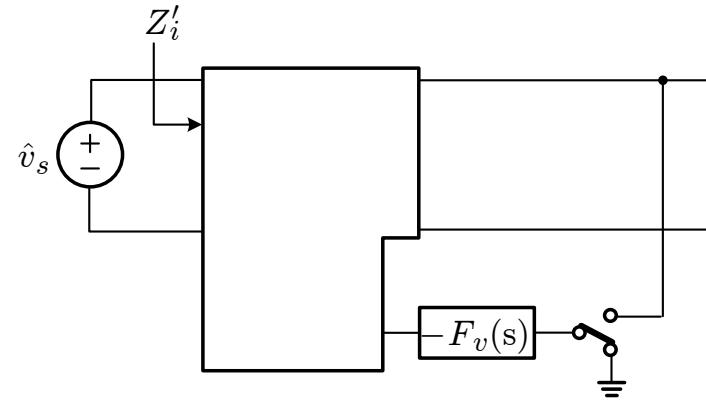

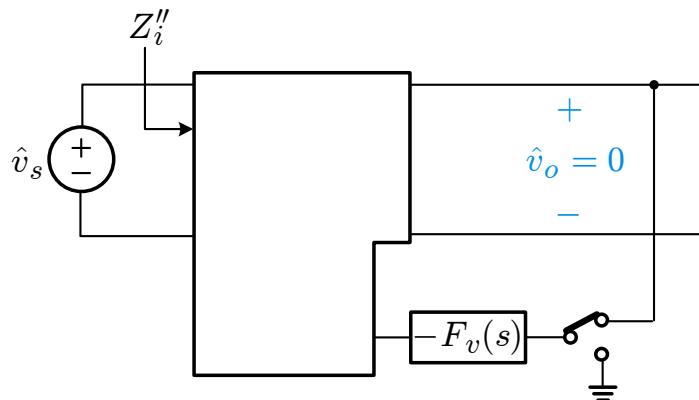$Z'_i$ : open-loop output-shorted input impedance







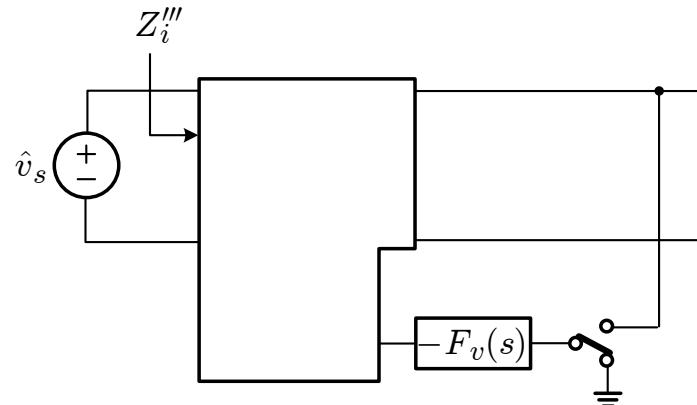$Z''_i$ : output-nullified input impedance




$Z'''_i$ : open-loop input impedance
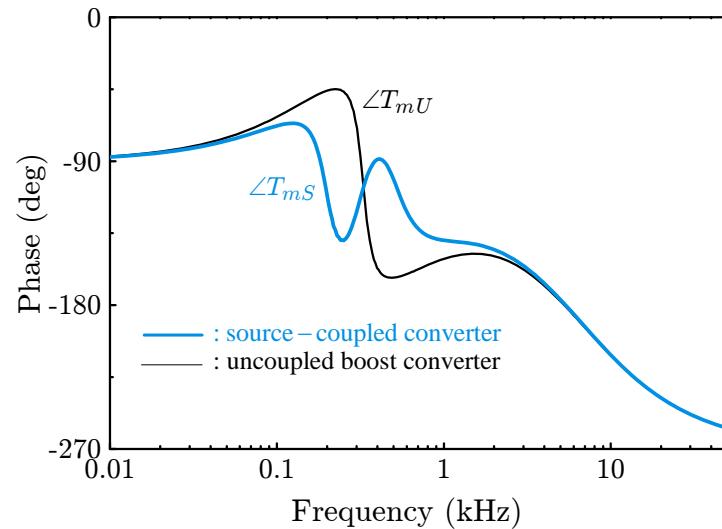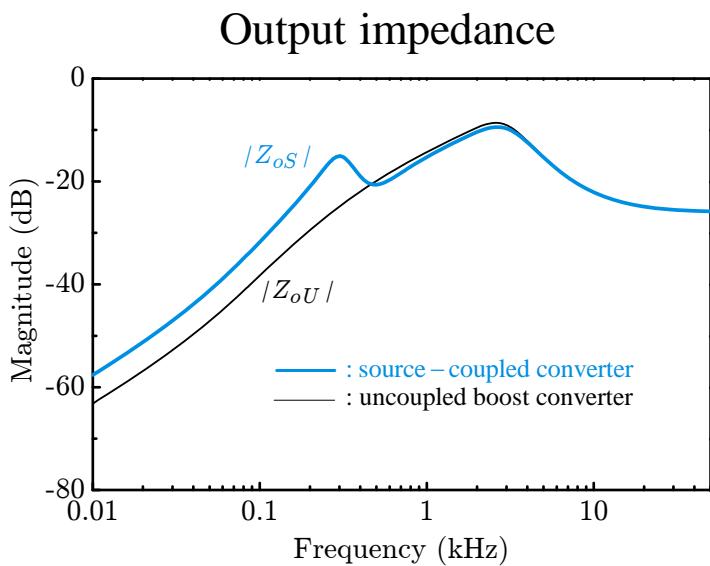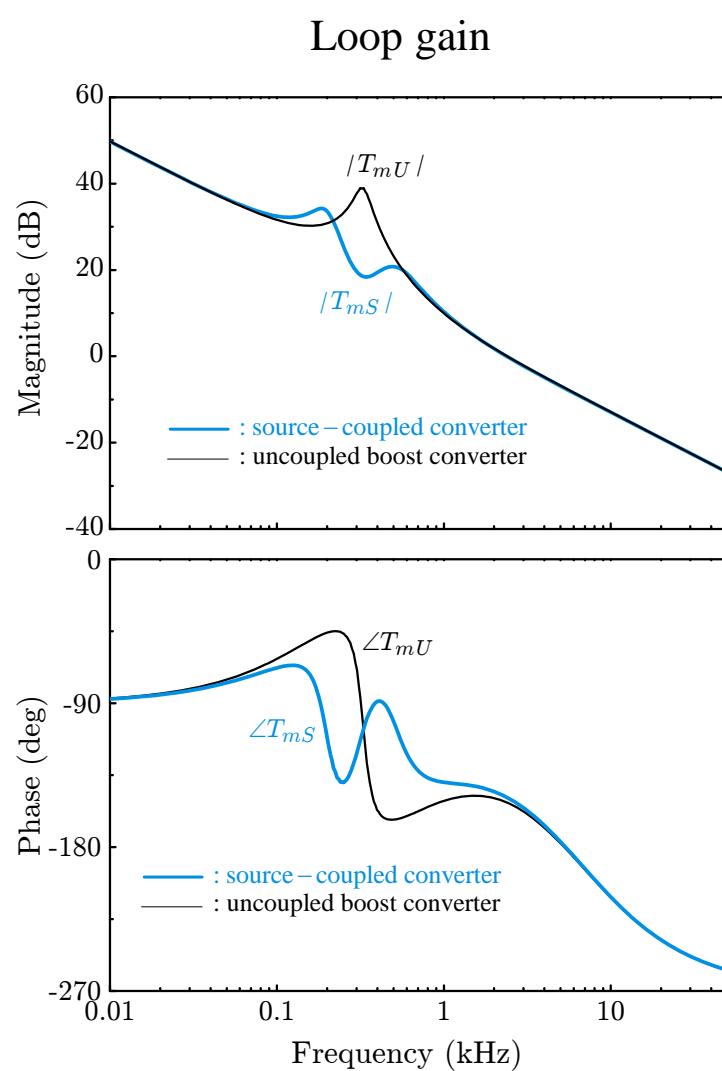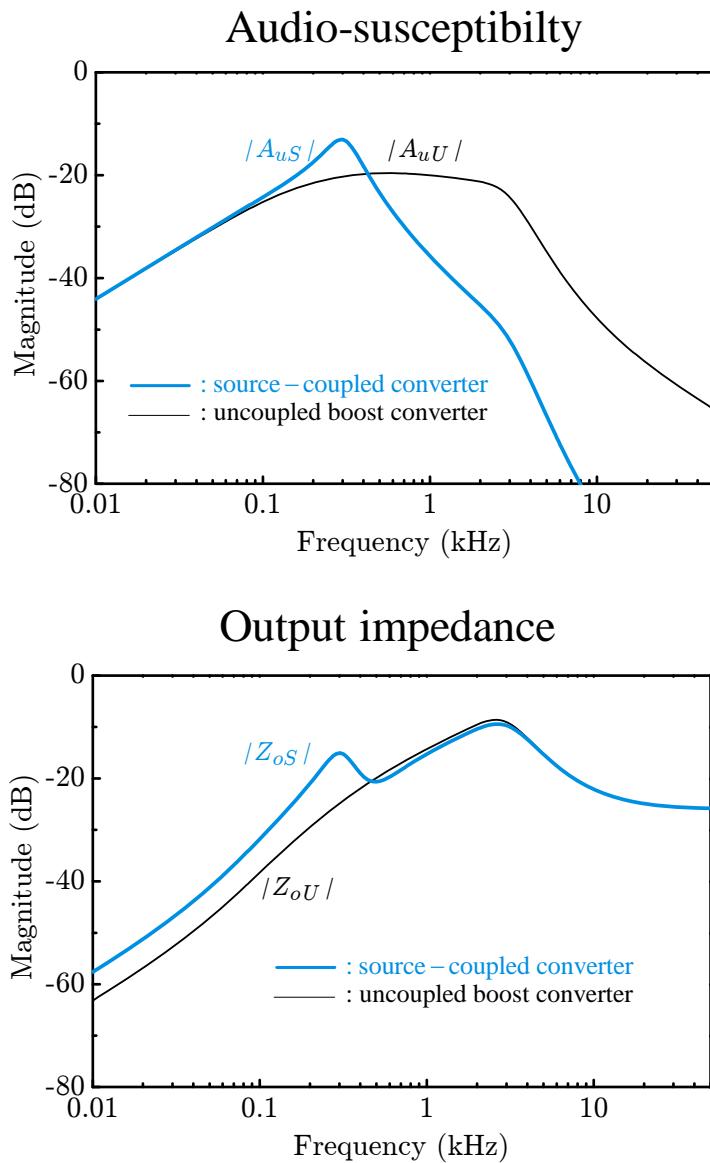
# Performance of Source-Coupled Boost Converter




# Source/Load-Coupled Converter

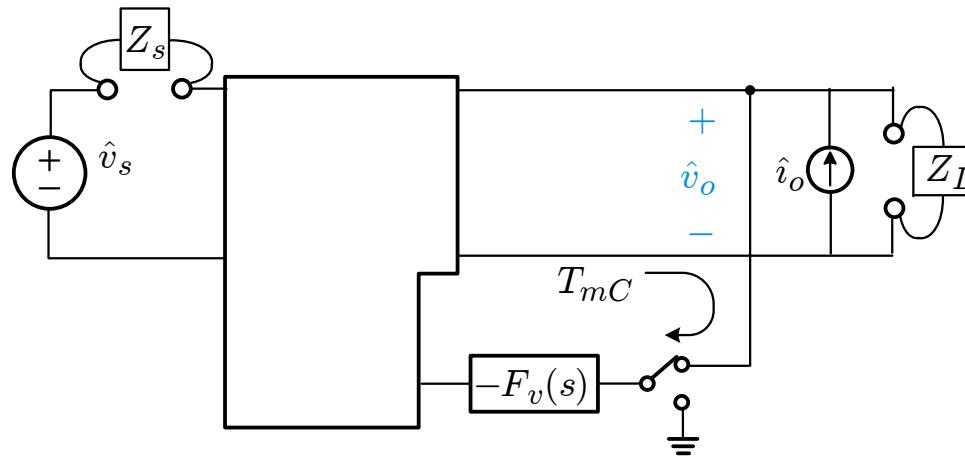

- Load-coupled converter:  $T_{mL}(s) = T_{mU}(s) \frac{1}{1 + (1 + T_{mU}(s)) \frac{Z_{oU}(s)}{Z_L(s)}}$
- Source/load coupled converter:

$$T_{mC}(s) = \left( T_{mU}(s) \frac{1}{1 + (1 + T_{mU}(s)) \frac{Z_{oU}(s)}{Z_L(s)}} \right) \begin{pmatrix} 1 + \frac{Z_s(s)}{Z_i''(s)} \\ 1 + \frac{Z_s(s)}{Z_i'''(s)} \end{pmatrix}$$

# Middlebrook's Feedback Theorem

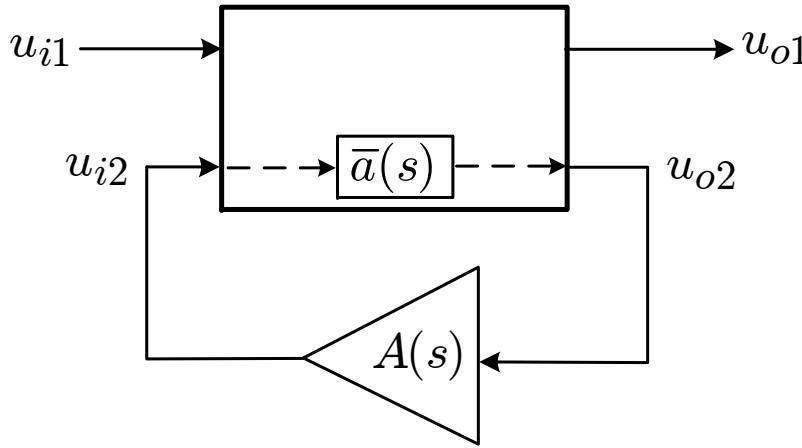

- Two-output feedback controlled system

$A(s)$ : feedback gain

$\bar{a}(s)$ : forward gain


- $$H(s) = \frac{u_{oi}(s)}{u_{i1}(s)} = H_\infty(s) \frac{T_m(s)}{1 + T_m(s)} + H_0(s) \frac{1}{1 + T_m(s)}$$

$H_\infty(s) = H(s)_{u_{o2}=0}$  : feedback-signal nullified transfer gain


$H_0(s) = H(s)_{A=0}$  : open loop transfer gain

$T_{mU}(s) = A(s)\bar{a}(s)$  : loop gain


# Pictorial Illumination

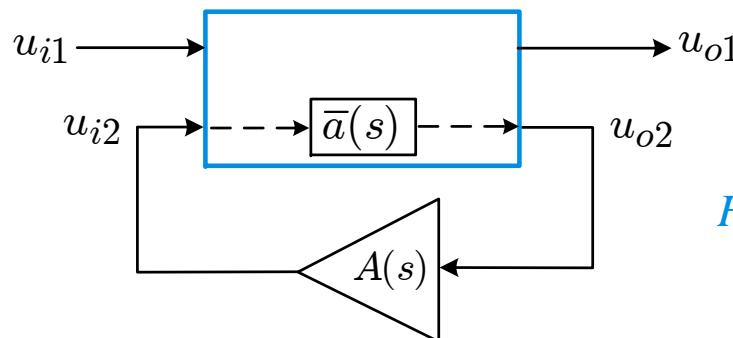

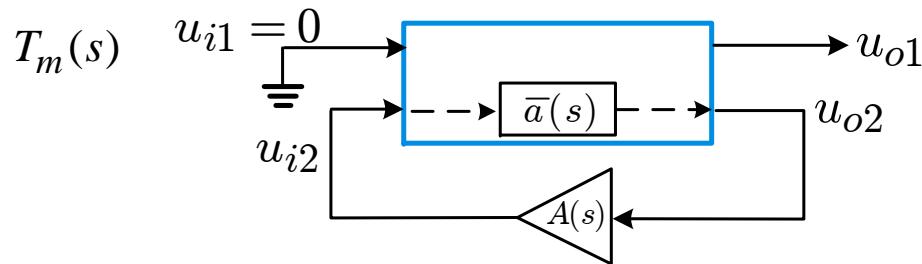
$$H(s) = H_\infty(s) \frac{T_m(s)}{1 + T_m(s)} + H_0(s) \frac{1}{1 + T_m(s)}$$



$$T_m(s) = A(s) \bar{a}(s)$$

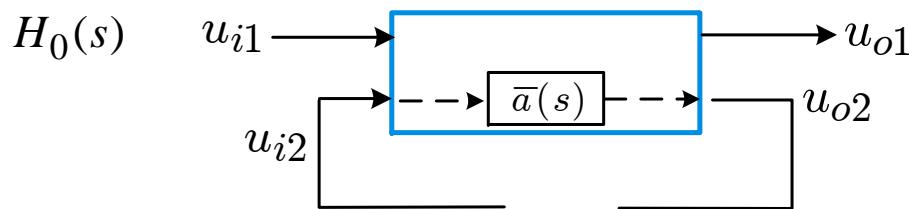


$$H_0(s) = \frac{u_{o1}(s)}{u_{i1}(s)} \Big|_{A(s)=0}$$

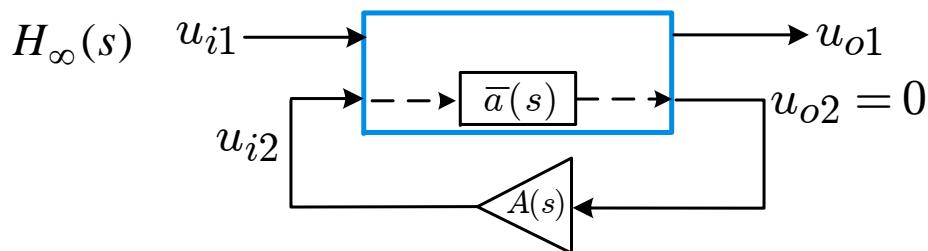


$$H_\infty(s) = \frac{u_{o1}(s)}{u_{i1}(s)} \Big|_{u_{o2}=0}$$

# Single-Output Feedback System

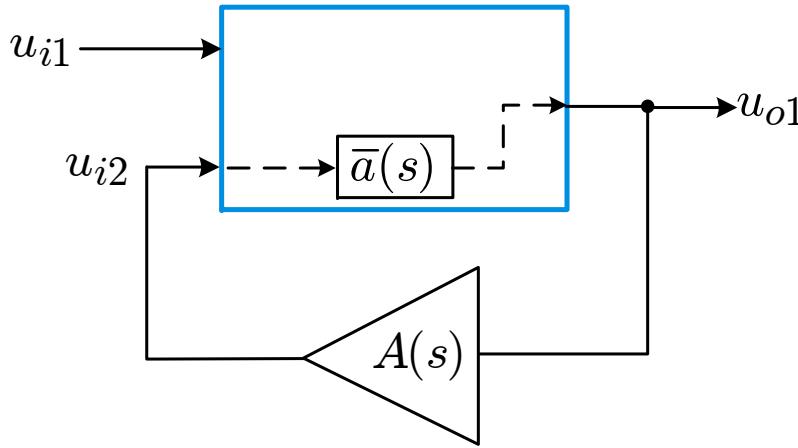

- $H(s) = \frac{u_{o1}(s)}{u_{i1}(s)} = H_\infty(s) \frac{T_m(s)}{1 + T_m(s)} + H_0(s) \frac{1}{1 + T_m(s)}$ 
$$H_\infty(s) = \frac{u_{o1}(s)}{u_{i1}(s)} \Big|_{u_{o1}(s)=0} = 0$$
- $H(s) = \frac{u_{o1}(s)}{u_{i1}(s)} = H_0(s) \frac{1}{1 + T_m(s)}$

# Input Impedance of Uncoupled Converter

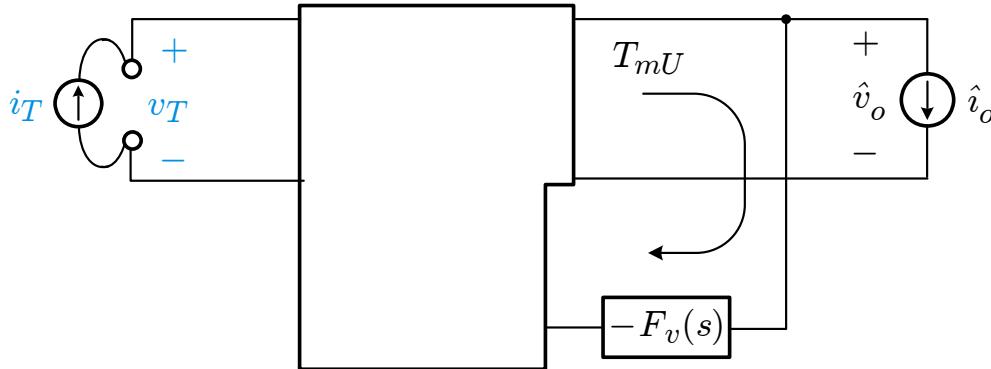

- $$\frac{1}{Z_{iU}(s)} = \frac{i_T(s)}{v_T(s)} = \frac{1}{Z''_i(s)} \frac{T_{mU}(s)}{1 + T_{mU}(s)} + \frac{1}{Z'''_i(s)} \frac{1}{1 + T_{mU}(s)}$$

$Z''_i(s)$ : output nullified input impedance

$Z'''_i(s)$ : open-loop input impedance

$T_{mU}(s)$ : loop gain

- $$Z_{iU}(s) \approx \begin{cases} Z''_i(s) & \text{for frequencies where } |T_{mU}| \gg 1 \\ Z'''_i(s)G_{vs}(s) & \text{for frequencies where } |T_{mU}| \ll 1 \end{cases}$$

# Chapter Summary

---

DC Power Distribution System

Uncoupled Converter

Power Stage Dynamics and Control Design of Uncoupled Converter

Coupled Converters and Middlebrook's Extra Element Theorem

Load-coupled converter

Source-coupled converter

Source/load-coupled converter

Middlebrook's Feedback Theorem