
 


Final Term Project

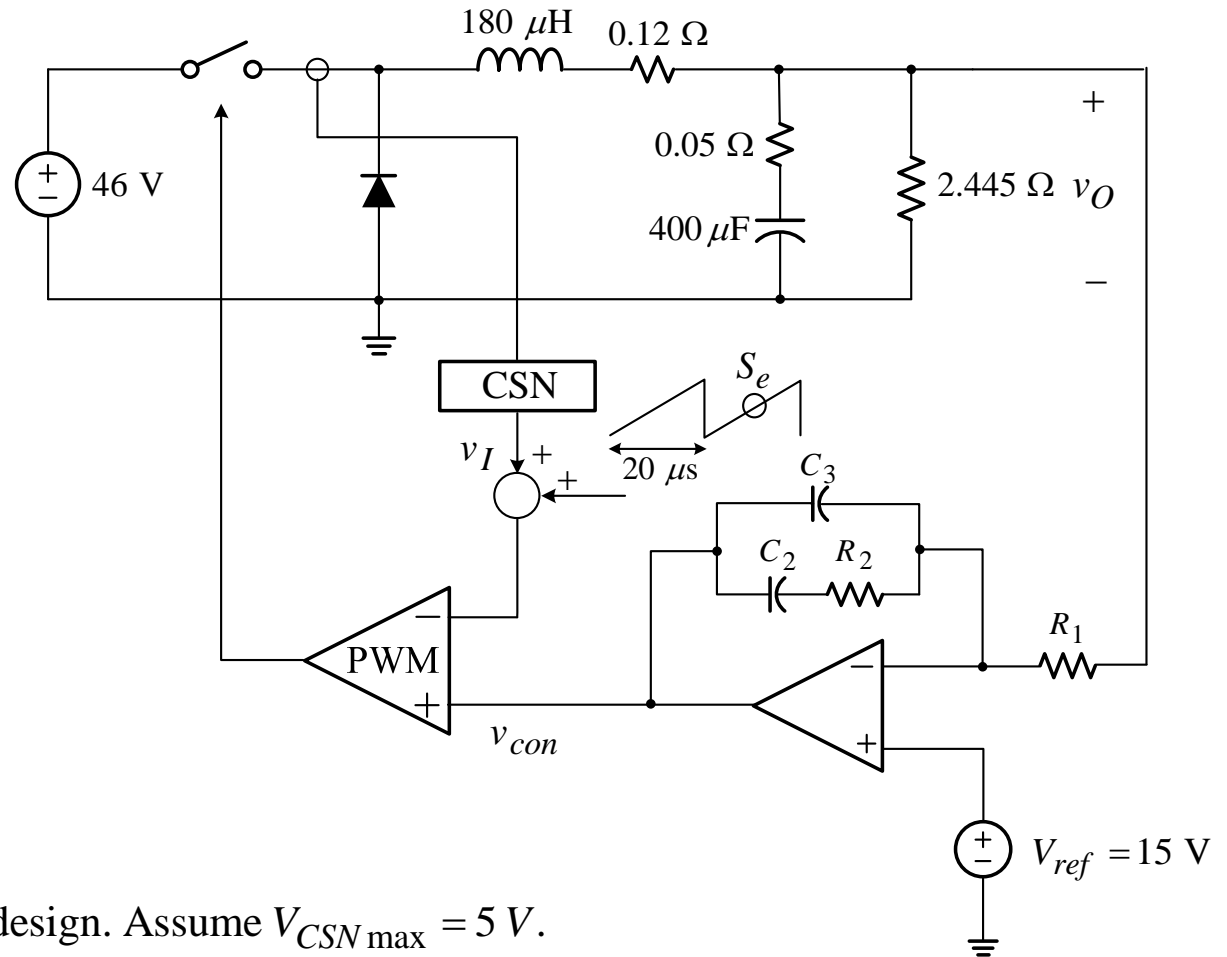Control Design and Performance Validation of Buck Converter




Buck Converter Design and Validation



- 1) Perform the current loop design. Assume $V_{CSN \max} = 5$ V.
- 2) Analyze and validate $G_{vci}(s)$ of the converter.

Buck Converter Design and Validation

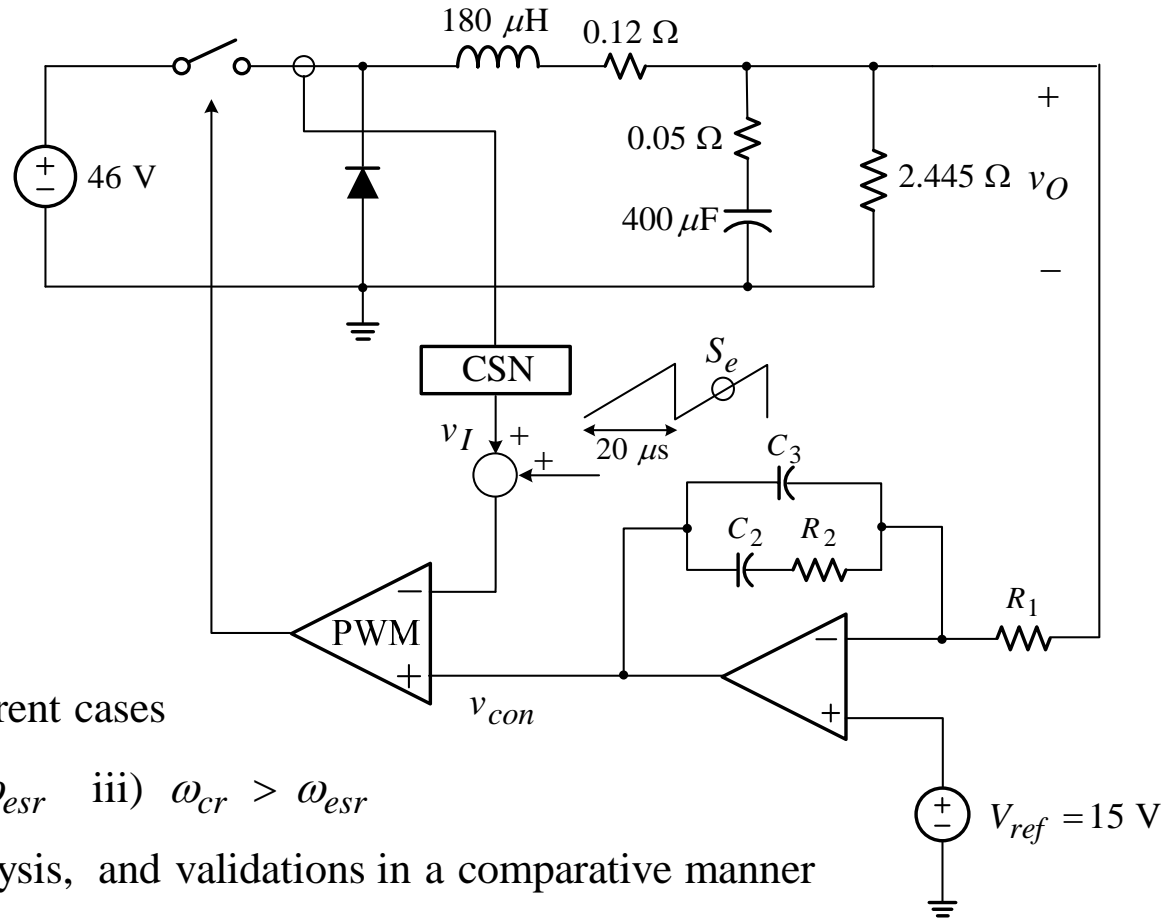


Consider the following three different cases

- i) $\omega_{cr} < \omega_{esr}$
- ii) $\omega_{cr} = \omega_{esr}$
- iii) $\omega_{cr} > \omega_{esr}$

Perform the following design, analysis, and validations in a comparative manner

- 3) Perform the voltage loop design and validation.
- 4) Perform the loop gain analysis and validation.
- 5) Perform the output impedance analysis and validation.
- 6) Perform the step load change response analysis and validation.

Asymptotic Plot of $G_{vci}(s)$


 


- $$G_{vci}(s) \approx K_{vs} \frac{\left(1 - \frac{s}{\omega_{rhp}}\right) \left(1 + \frac{s}{\omega_{esr}}\right)}{\left(1 + \frac{s}{\omega_{pl}}\right) \left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2}\right)}$$


- The double pole at half the switching frequency introduces a peaking of $20 \log Q_p$.

$G_{vci}(s)$ Validation

Gvci_CMC_Buck

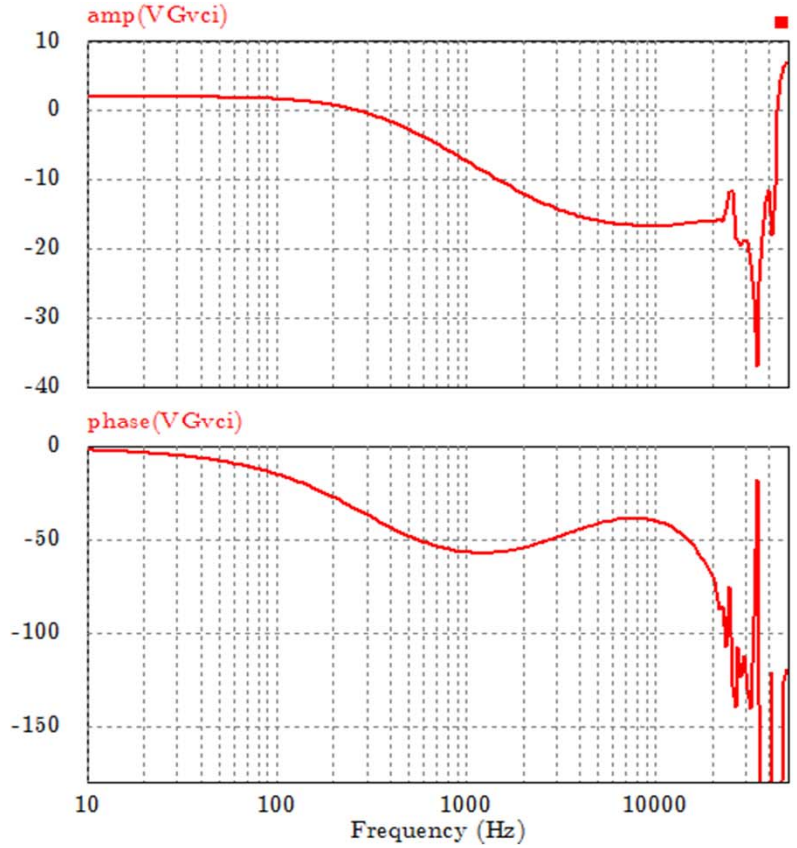
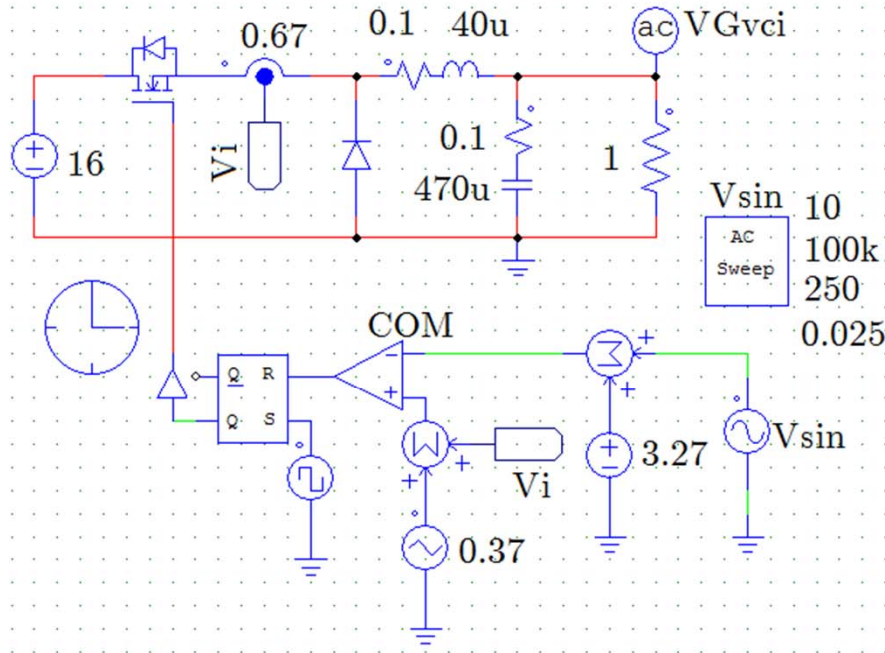


Loop Gain Asymptotic Plot

 


- $$T_m(s) = G_{vci}(s) F_v(s) = K_{vc} \frac{\left(1 - \frac{s}{\omega_{rhp}} \right) \left(1 + \frac{s}{\omega_{esr}} \right)}{\left(1 + \frac{s}{\omega_{pl}} \right) \left(1 + \frac{s}{Q_p \omega_n} + \frac{s^2}{\omega_n^2} \right)} \frac{K_v \left(1 + \frac{s}{\omega_{zc}} \right)}{s \left(1 + \frac{s}{\omega_{pc}} \right)}$$

Loop Gain Validation

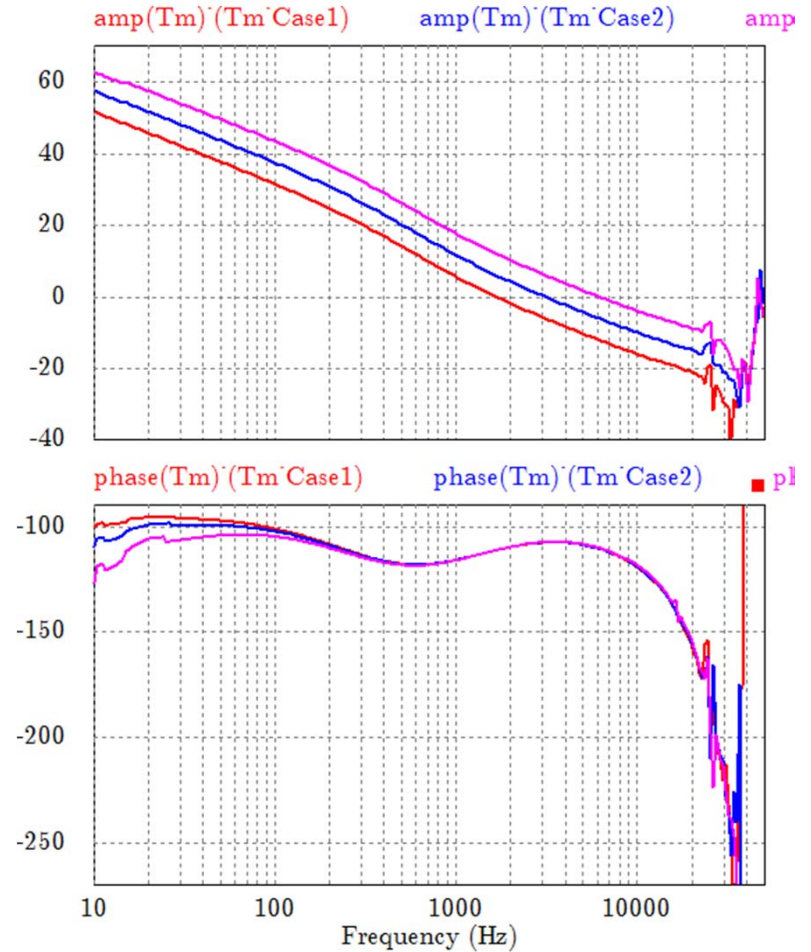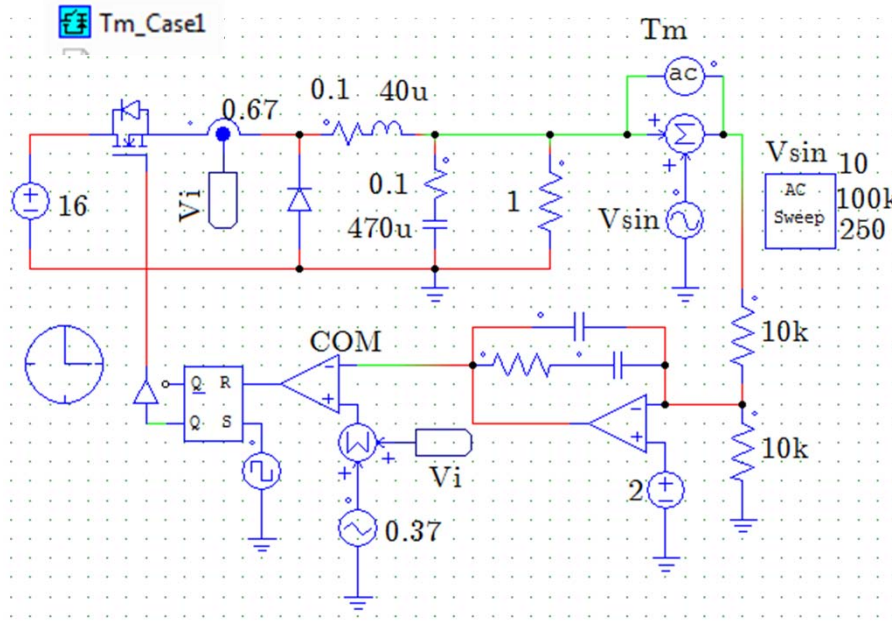

Output Impedance Analysis


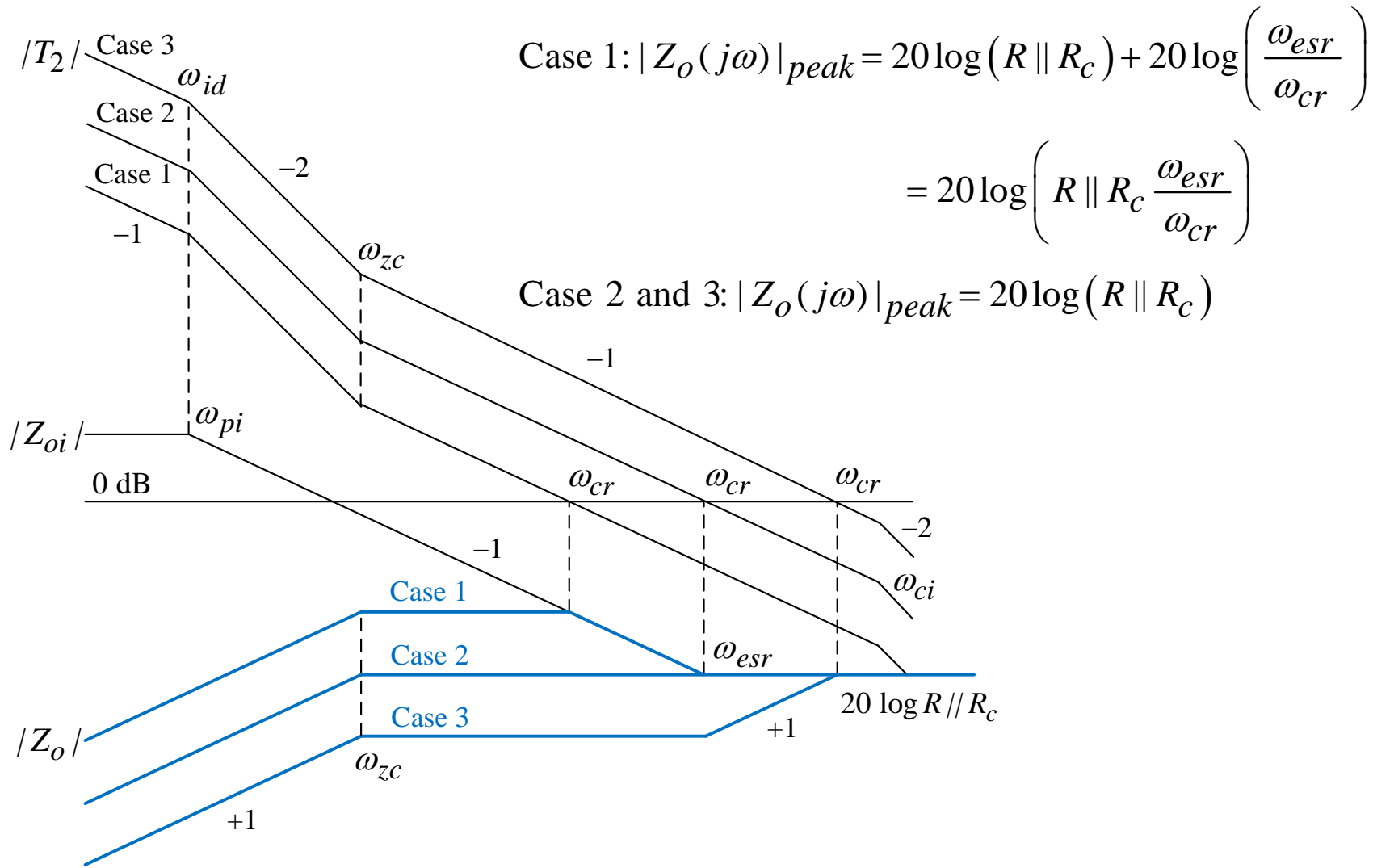


Case 1: $\omega_{cr} < \omega_{esr}$

Case 2: $\omega_{cr} = \omega_{esr}$

Case 3: $\omega_{cr} > \omega_{esr}$

Output Impedance Validation

 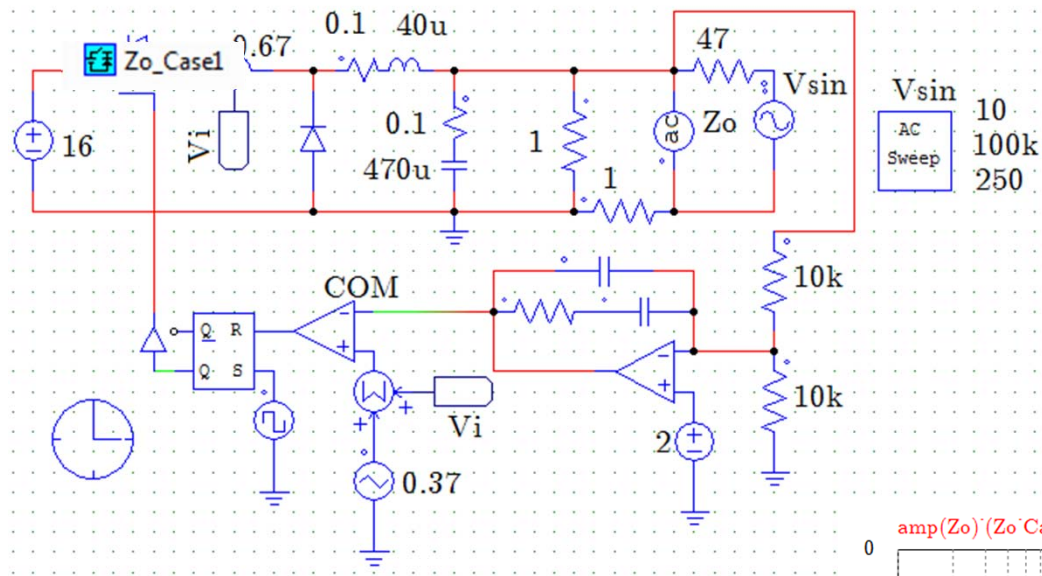

Step Load Response Validation

