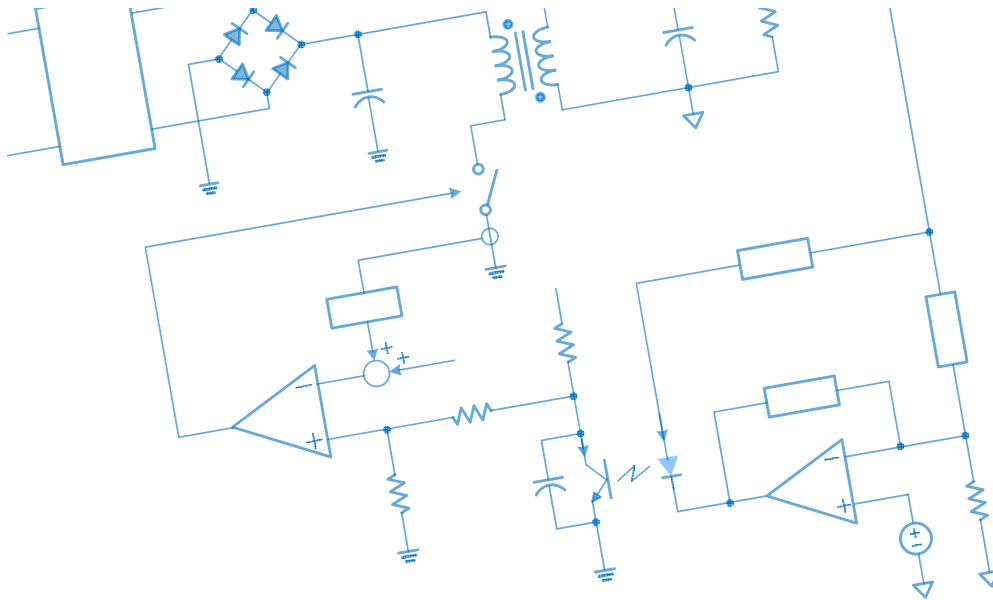


POWER ELECTRONICS with

PULSEWIDTH MODULATED DC-TO-DC POWER CONVERSION



POWER ELECTRONICS

- General Information

Office: IT3-314 Office Hour: Fri 9:00-12:00 AM Email: bchoi@ee.knu.ac.kr


Home Page: [http:// smpc.knu.ac.kr](http://smpc.knu.ac.kr)

OCW Site: <http://bkict-ocw.knu.ac.kr>

- Course Objective: As an introductory course in power electronics, the class will address basic principles, analysis techniques, and applications of modern power electronics with a strong emphasis on switchmode dc-to-dc power conversions. The students would learn methods of solving various power electronics problems using their knowledge about electronics, circuit theories, and control theories.
- Text: *Byungcho Choi*, "Fundamentals of PWM Power Conversion, 2nd Ed., Guardian Book Publishing
- Grading Policy:
 - Midterm Test: 45 %, Final Exam: 45 %, Class Activities: 10 %


Tentative Course Outline

Topic	Major Contents	Weeks
Chapter 1: PWM Dc-to-Dc Power Conversion Chapter 2: Power Stage Components	<ul style="list-style-type: none"> • Introduction to PWM dc-to-dc power conversion • Semiconductor switches and switching circuits • Energy storage/transfer devices and switching circuits • Switch circuits in practice 	2 weeks
Chapter 3: Buck Converter	<ul style="list-style-type: none"> • Basic principles of buck converter • Time-domain analysis of buck converter • Discontinuous-conduction mode of operation • Closed-loop control of buck converter 	2 weeks
Chapter 4: Dc-to-Dc Power Converter Circuits	<ul style="list-style-type: none"> • Boost converter • Buck/boost converter • Flyback converter • Isolated converter topologies 	2 weeks
Midterm Test		
Chapter 5: Modeling PWM Dc-to-Dc Converters Chapter 6: Power Stage Transfer Functions	<ul style="list-style-type: none"> • Averaging power stage dynamics • Linearizing averaged power stage dynamics • Bode plot for transfer functions • Power stage dynamics of three basic converters 	3 weeks
Chapter 7: Dynamic Performance of PWM Dc-to-Dc Converters Chapter 8: Closed-Loop Performance and Feedback Design	<ul style="list-style-type: none"> • Frequency-domain performance of dc-to-dc converters • Time-domain performance of dc-to-dc converters • Stability of dc-to-dc converters • Compensation design and closed-loop analysis 	4 weeks
Final Exam		

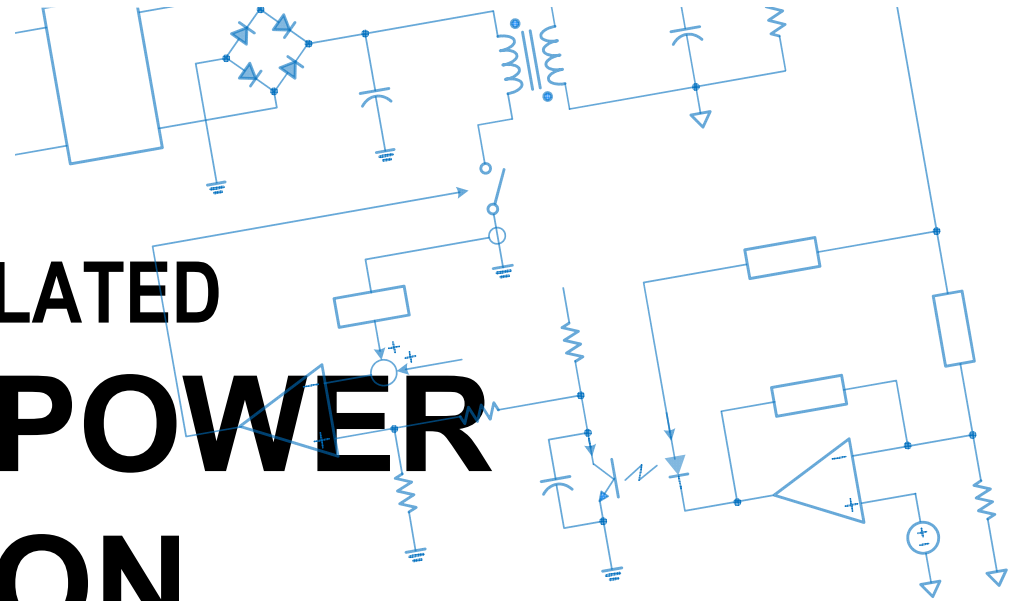

PULSEWIDTH MODULATED DC-TO-DC POWER CONVERSION

Circuits, Dynamics, and Control Designs

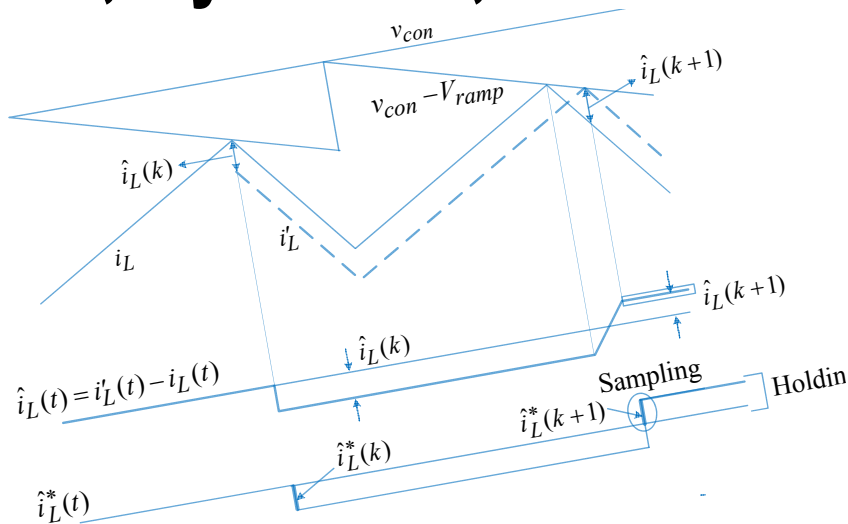

Contents in Brief

Part One : Circuits for Dc-to-Dc Conversion

Chapter 1: PWM Dc-to-Dc Power Conversion

Chapter 2: Power Stage Components

Chapter 3: Buck Converter

Chapter 4: Dc-to-Dc Power Converter Circuits

Part Two: Modeling, Dynamics, and Design of PWM Dc-to-Dc Converters

Chapter 5: Modeling PWM Dc-to-Dc Converters

Chapter 6: Power Stage Transfer Functions

Chapter 7: Dynamic Performance of PWM Dc-to-Dc Converters

Chapter 8: Closed-Loop Performance and Feedback Compensation

**Chapter 9: Practical Considerations in Modeling, Analysis, and Design of
PWM Converters**


Part Three : Current Mode Control

Chapter 10: Current Mode Control-Functional Basics and Classical Analysis

**Chapter 11: Current Mode Control-Sampling Effects and New Control Design
Procedures**

Chapter 1

PWM Dc-to-Dc Power Conversion

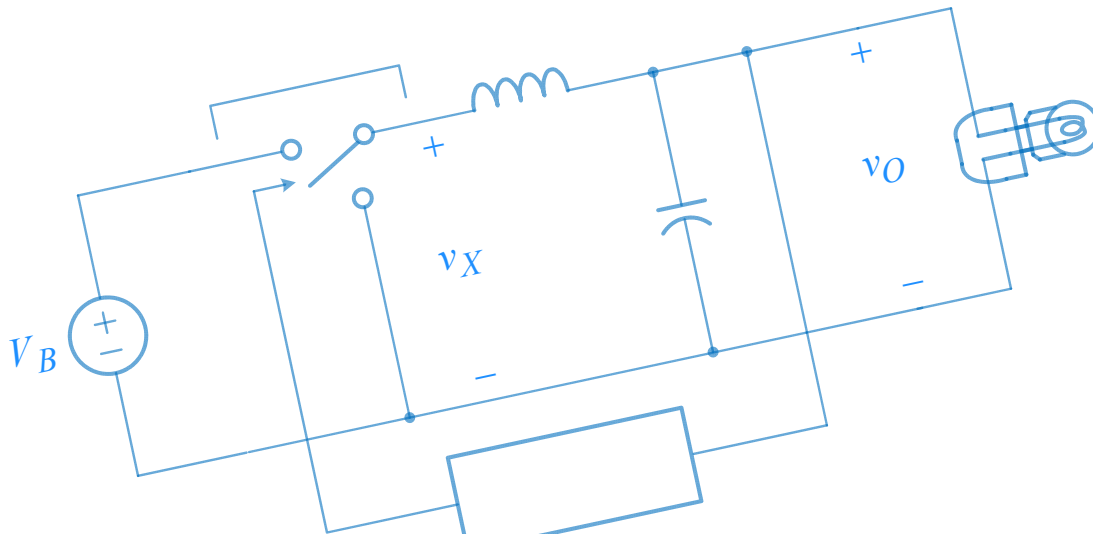

Chapter Outline

1) PWM Dc-to-Dc Power Conversion

Dc-to-Dc Power Conversion

PWM Technique

2) Dc-to-Dc Power Conversion System

3) Features and Issues of PWM Dc-to-Dc Converter


Electric Bulb Drive Circuit

- Energy source and load

Source: battery with variable output voltage ($V_B = 18 \text{ V} - 30 \text{ V}$)

Load: 12 V electric bulb ($V_O = 12 \text{ V}$)


- Conventional resistive solution

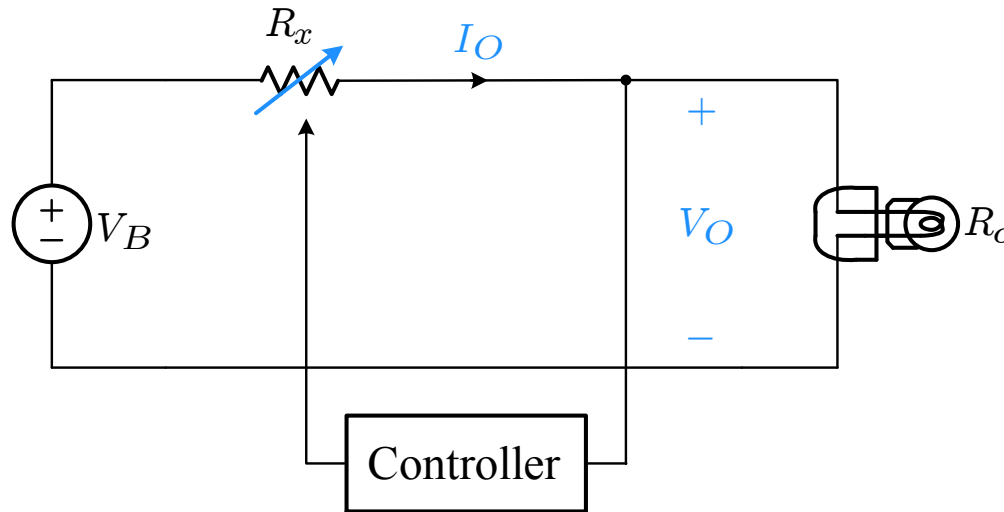

Control law:
$$V_O = \frac{R_o}{R_x + R_o} V_B = 12 \text{ V}$$

Ohmic loss at R_x :
$$P_{loss} = P_{in} - P_{out} = I_O V_B - I_O V_O \\ = I_O (V_B - V_O)$$

Problem of Resistive Solution

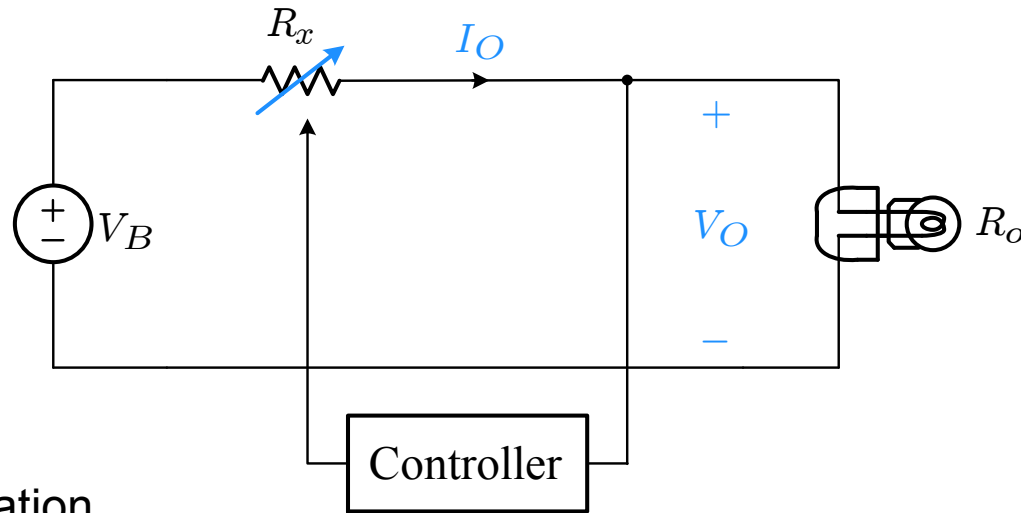

- Efficiency evaluation

Assumptions

Battery voltage: $V_B = 30 \text{ V}$

Bulb: 60 W power at 12 V voltage level $\Rightarrow V_O = 12 \text{ V}$ and $I_O = 60 / 12 = 5 \text{ A}$

$$P_{loss} = I_O(V_B - V_O) = 5(30 - 12) = 90 \text{ W}$$


$$\text{Efficiency: } \eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}} = \frac{60}{60 + 90} = 0.4$$

- Consequence of poor efficiency

Heat generation \Rightarrow Requirement of cooling system



\Rightarrow Increase in weight and size of bulb drive circuit

SPDT Switch

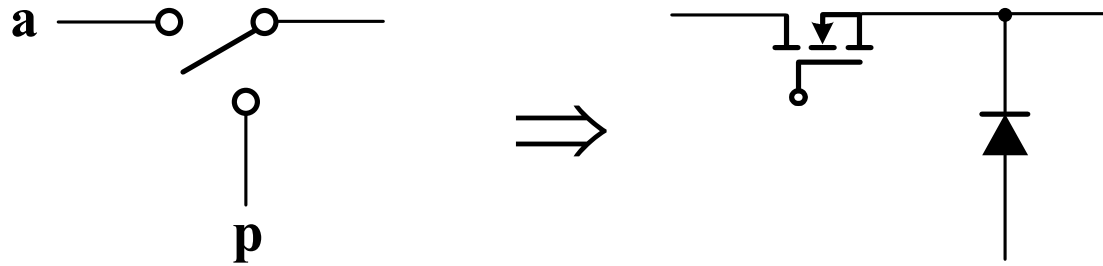


- Single-pole double-throw (SPDT) switch contains one pole which is always connected to one of the two contacts: the **throw a** and the **throw p**.
- SPDT switch is usually implemented using **MOSFET-diode pair**.

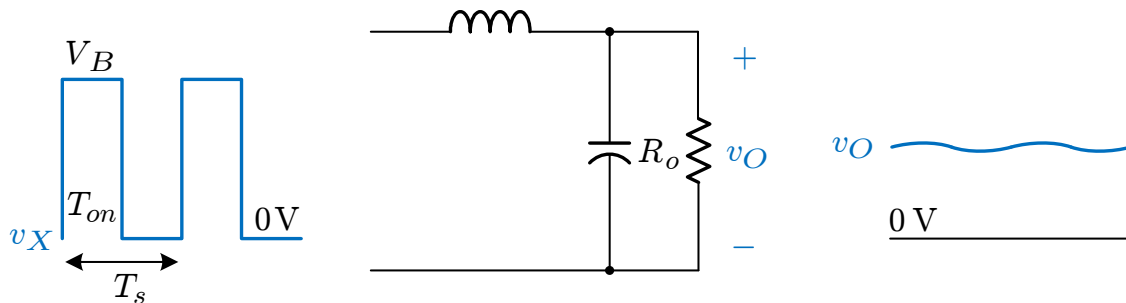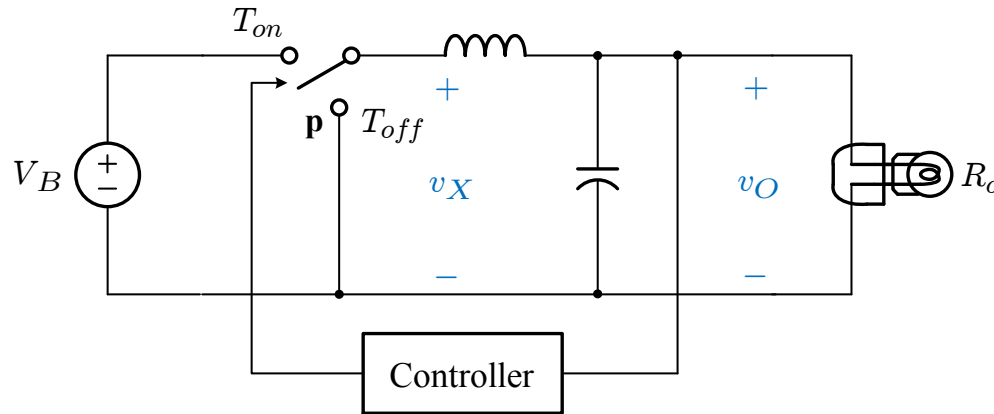Dc-to-Dc Power Conversion as Alternative Solution



- Two steps in dc-to-dc power conversion
 - i) conversion of dc voltage into a pulse waveform
 - ii) filtering of the pulse waveform into another dc voltage
- Control law: $v_O(t) \approx V_O = \text{average} \{v_X(t)\} = \bar{v}_X(t) = \frac{T_{on}}{T_s} V_B = 12 \text{ V}$
- No power loss in circuit $\Rightarrow \eta = 100 \%$

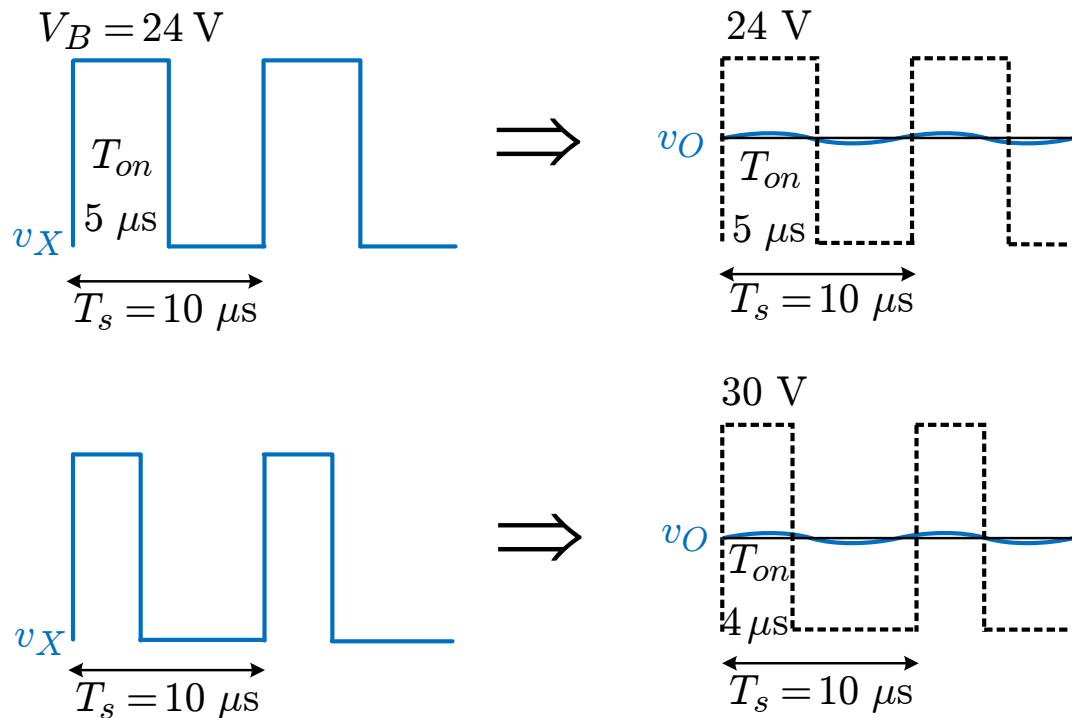Pulsewidth Modulation for Output Voltage Regulation




- Control law: $\frac{T_{on}}{T_s} V_B = \frac{T'_{on}}{T_s} V'_B = 12\text{ V}$
- Output remains constant in spite of input voltage variation
 \Rightarrow Output voltage regulation using **pulsewidth modulation** (PWM) scheme


PWM Dc-to-Dc Converter

- Power conversion: changing electrical energy/power from one form to another form using electric devices
- Power electronics: electronic engineering that deals with all types of power conversions *while questing the maximum possible conversion efficiency*
- Dc-to-dc power conversion: process of changing the voltage level of a dc source to another value
- PWMdc-to-dc power converter: dc-to-dc conversion circuit operating under the PWM technique

Classification of Power Conversion

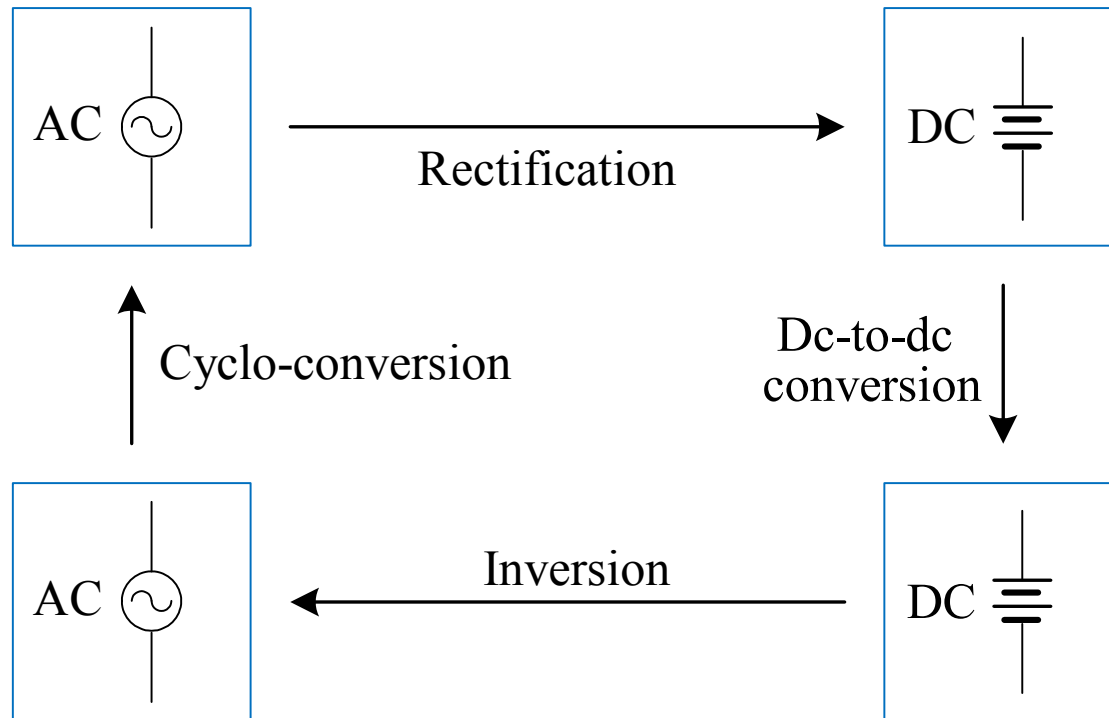


Dc-to-Dc Power Conversion System

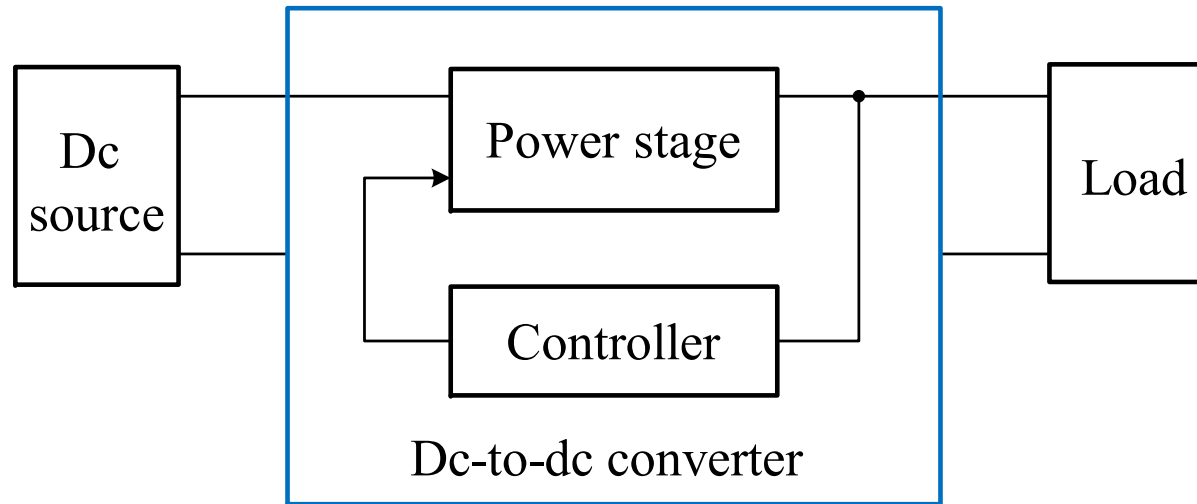

- Dc source with non-ideal characteristics
 - Standalone dc source: variation in source voltages
 - Rectified ac source: ac ripple and noise components
- Load as a dynamic current sink with general impedance characteristics
 - Electric equipment: non-resistive load impedance characteristics
 - Digital logic system: dynamic changes in load current

Dc-to-Dc Power Conversion System

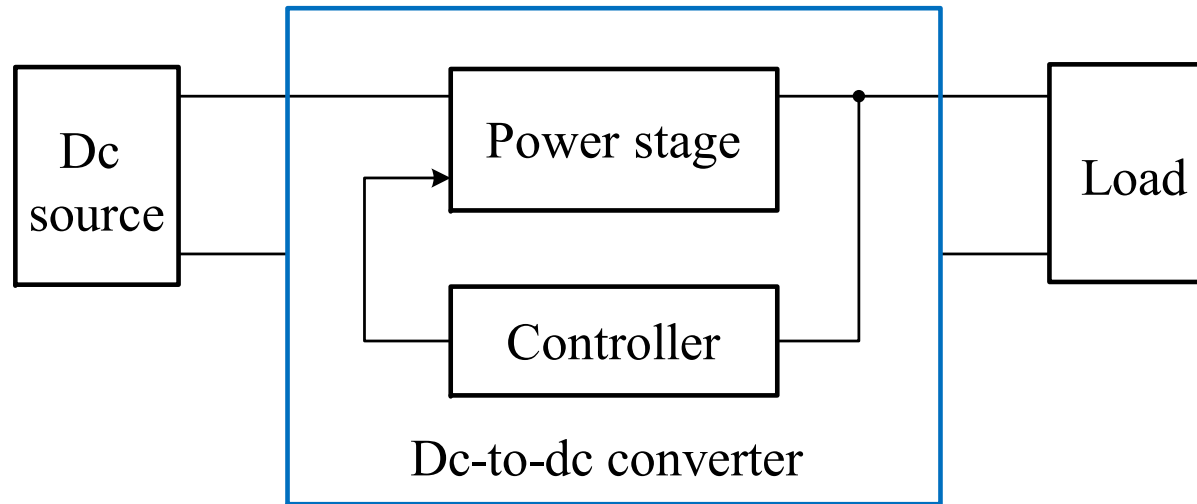

- Dc-to-dc converter as a voltage source

Functions of dc-to-dc converter: power conversion and energy flow control

- Components of dc-to-dc converter

Power stage: semiconductor switches – MOSFETs and diodes
energy storage/transfer devices – inductors, capacitors,
and transformers

Controller: ICs and discrete components

Features and Issues of PWM Dc-to-Dc Converter

- Power stage components

Semiconductor devices: high-frequency switching operations

Inductors and capacitors: periodic voltage/current excitations

Transformers: periodic voltage/current excitations

- Power stage configurations

Accommodation of input voltage and load current requirements

Very large or small voltage conversion ratio

Galvanic isolation between source and load

- Dynamic modeling and analysis

Closed-loop feedback control for output regulation

Stability and dynamic performance

Dynamic modeling to embrace conventional analysis techniques

- Dynamic performance and control design

Dynamic performance: stability, transfer functions, and transient responses

Feedback control design for optimal dynamic performance